




# Applying SEL Differential Relays

## Introduction to Transformer Differential Protection

# Transformer Differential Protection Presentation Objectives

- Explain challenges of transformer differential protection
- Understand need for tap, phase, and zero-sequence compensation and how they work
- Understand how transformer differential relays are made secure for inrush and overexcitation
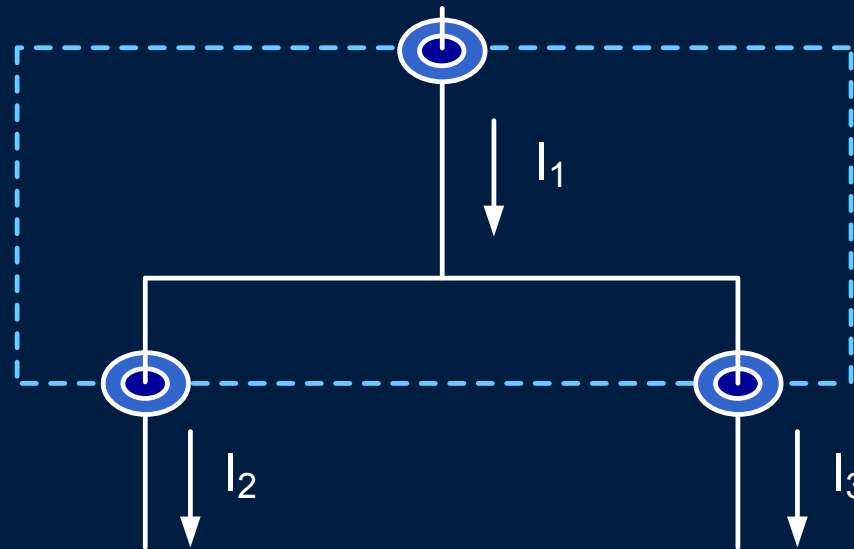
# Differential Protection is Easy in Theory




Kirchhoff's Current Law (KCL):  $\sum_{k=1}^n I_k = 0$


# Challenges to Transformer Differential Protection

- Current magnitude mismatch
- Phase shift across transformer
- Zero-sequence sources
- Energization inrush
- Overexcitation
- Unequal CT performance

# Differential Protection Principle

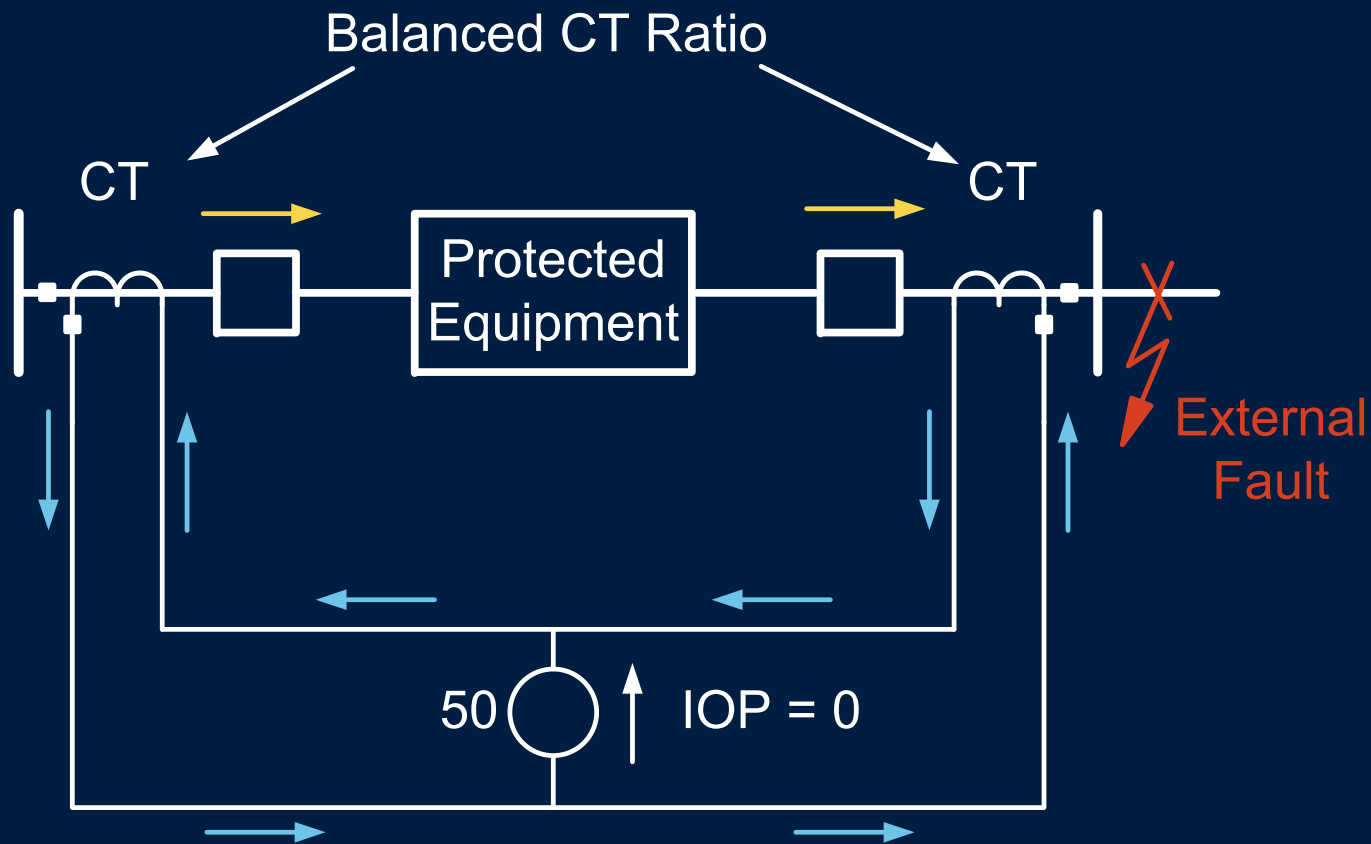


# Differential Protection Principle

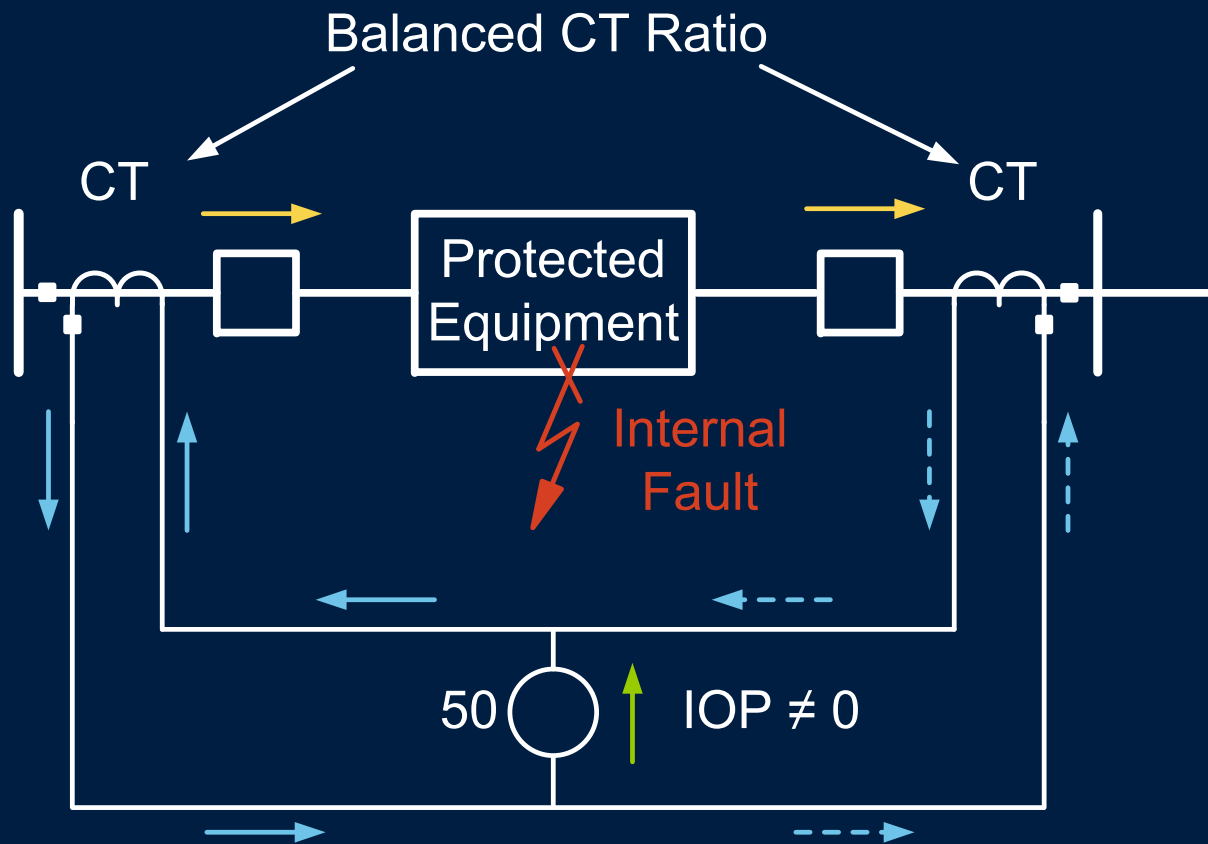

# **Current Magnitude and Phase Angle Difference Compensation**

# ANSI Transformer Connections


## DABY or Dy1

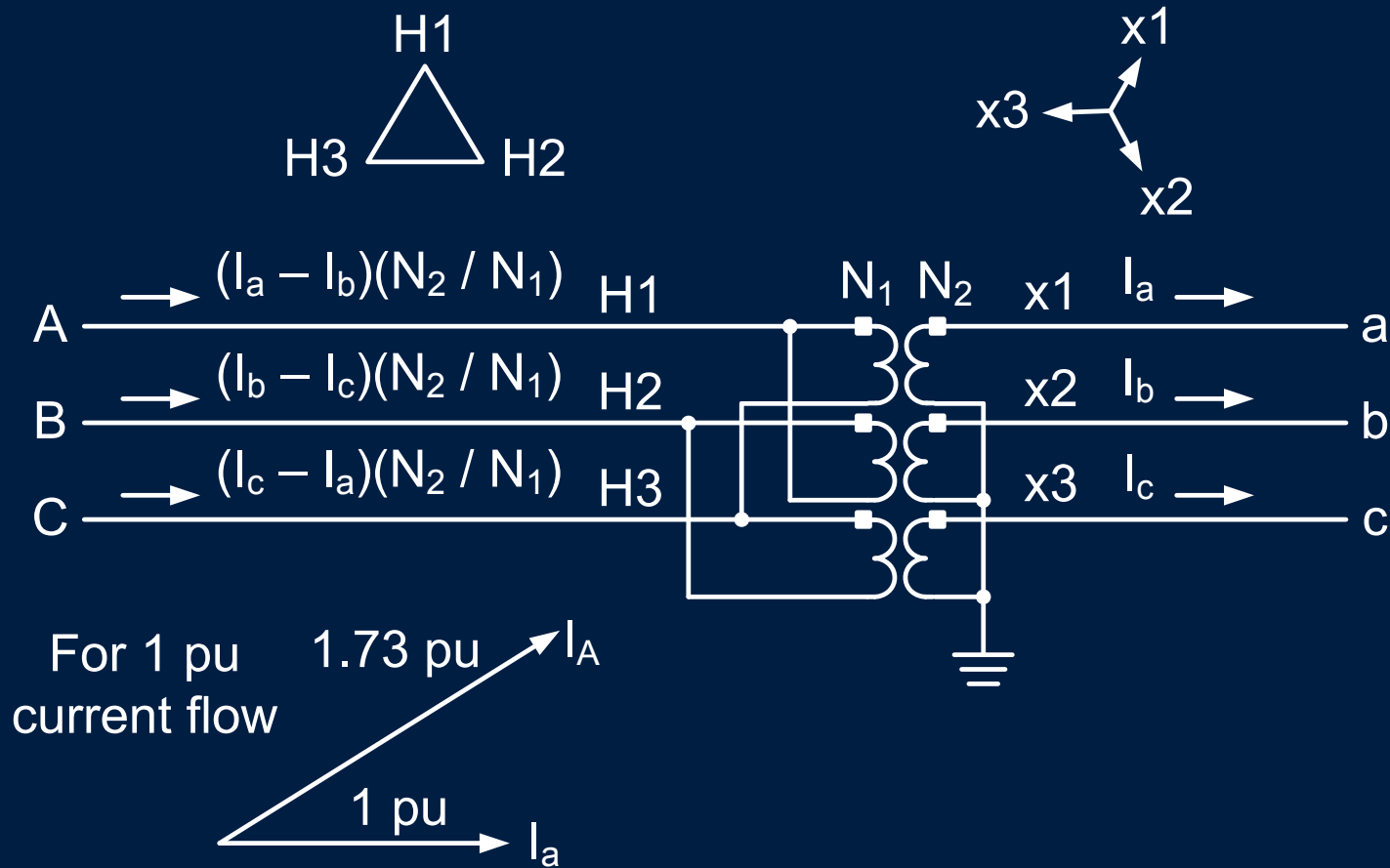




# ANSI Transformer Connections


## YDAC or Yd1

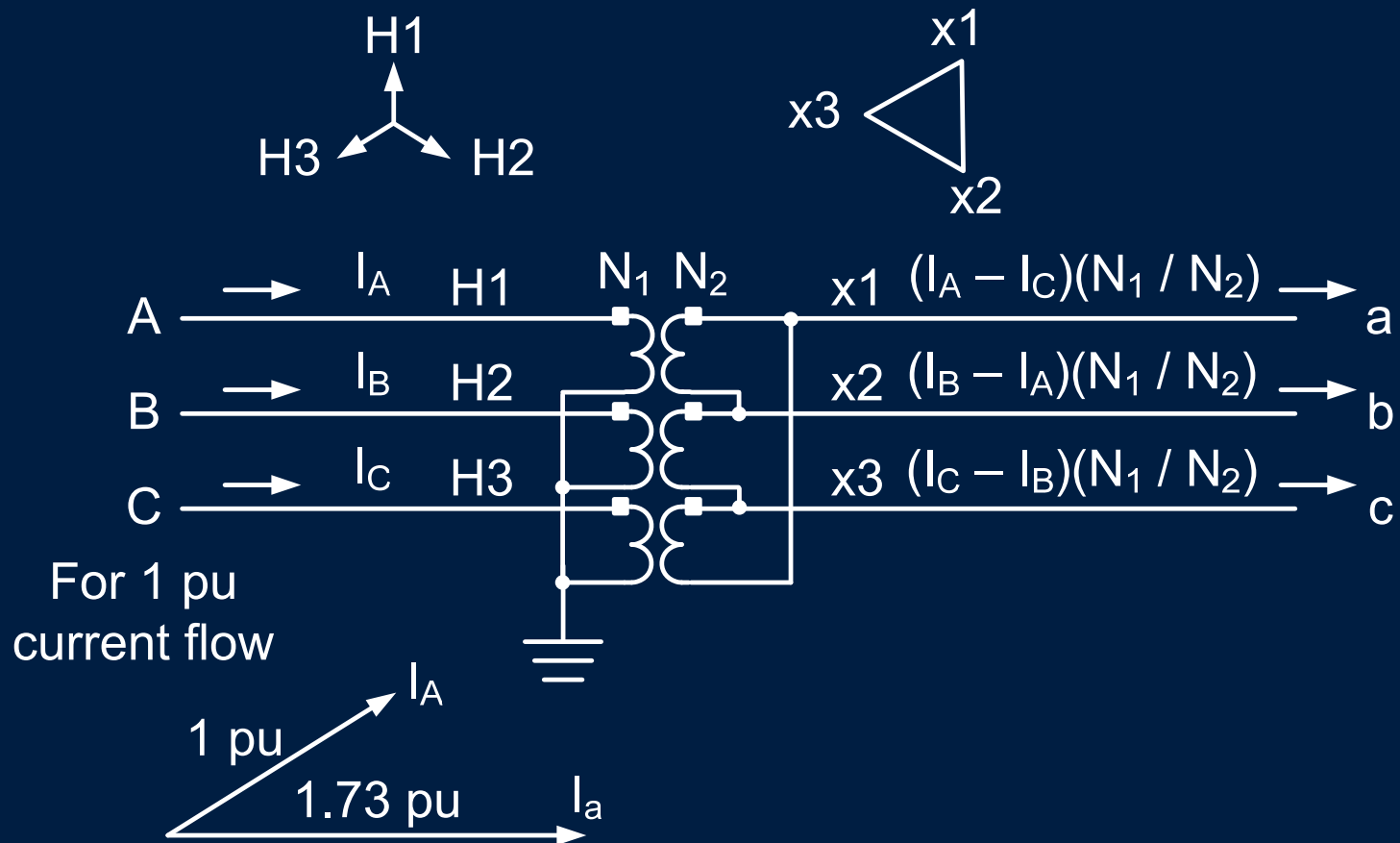


# Secondary Currents

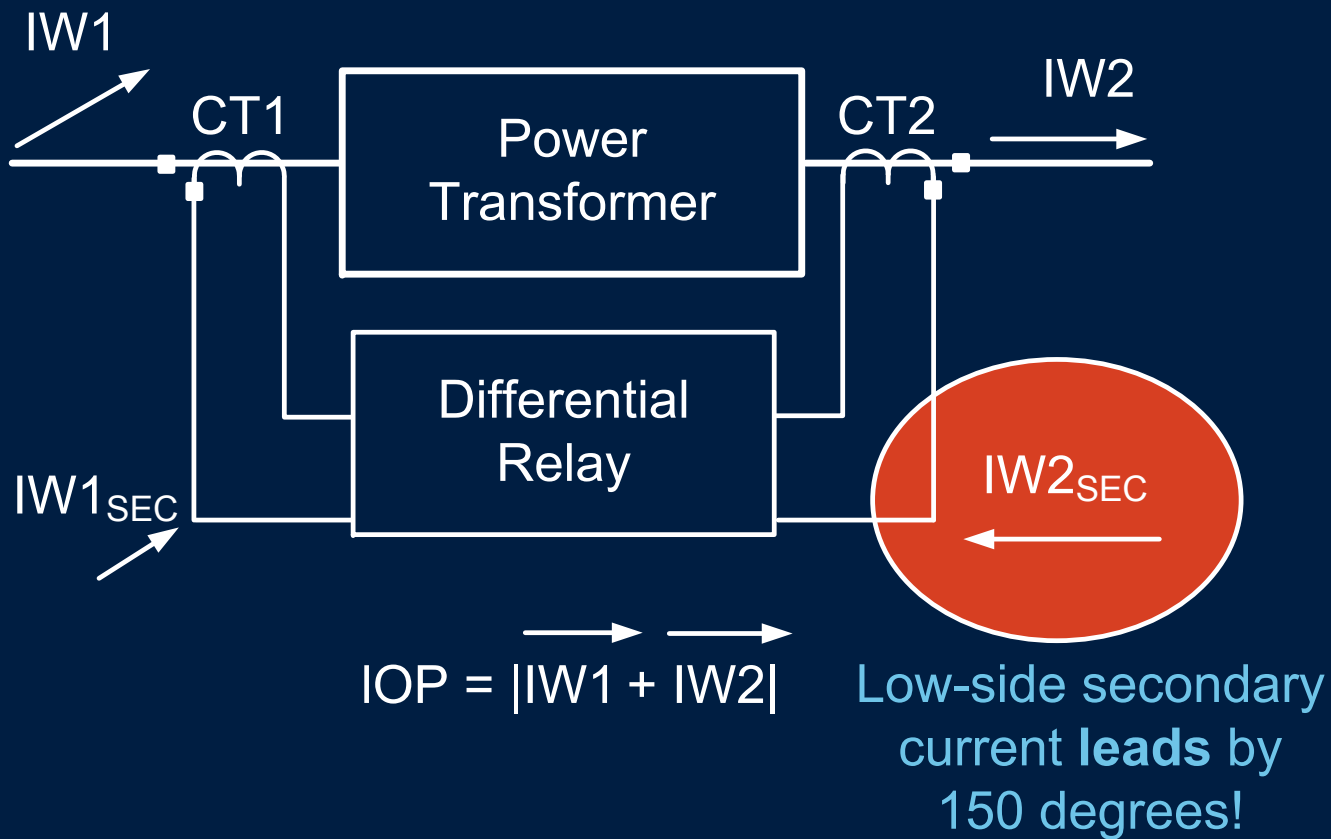

# Result of Uncompensated Phase Shift

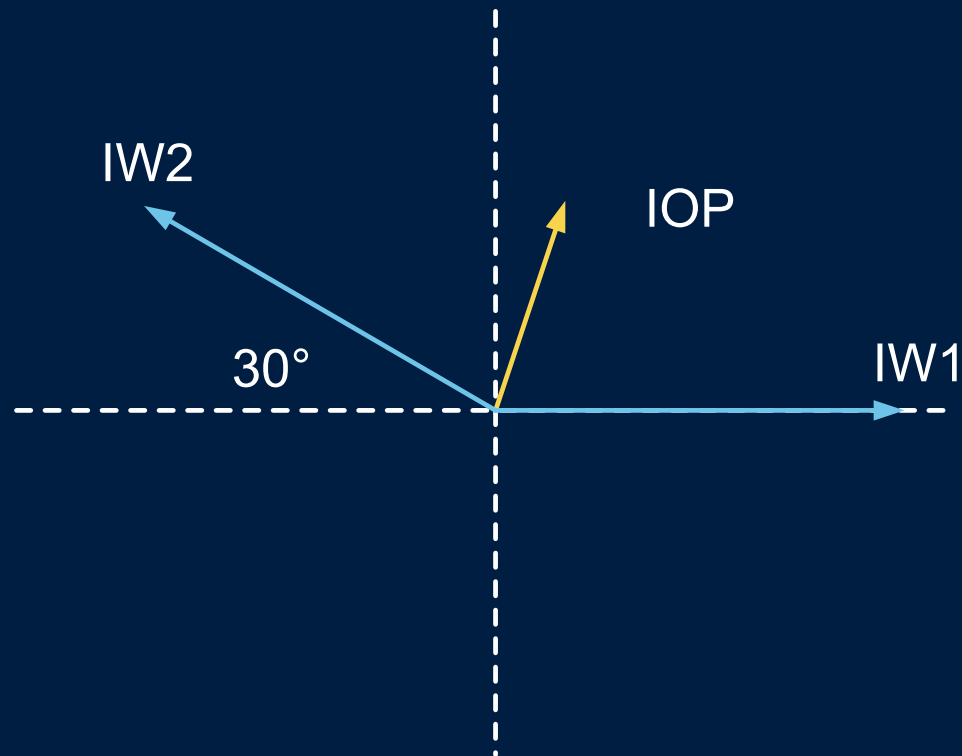

# Traditional Compensation

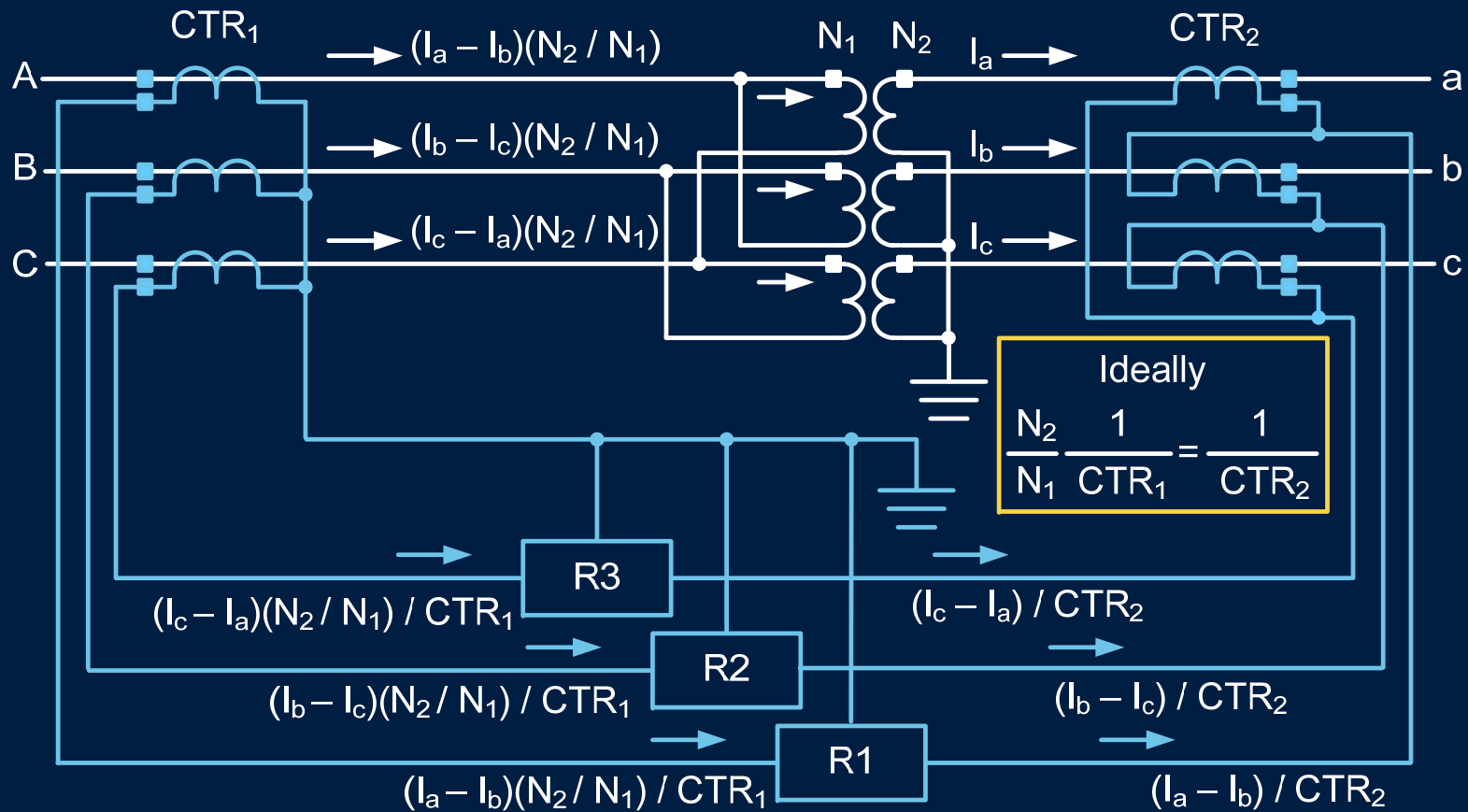

## CTR<sub>1</sub> and CTR<sub>2</sub> Ideal Relationship

$$\frac{N_2}{N_1} \frac{1}{CTR_1} = \frac{1}{CTR_2} \Rightarrow$$

$$\frac{N_1}{N_2} CTR_1 = CTR_2 \Rightarrow$$

$$CTR_2 = \sqrt{3} \frac{kV_1}{kV_2} CTR_1$$

Not always possible with standard CT ratios

## Compensation With Relays

- EM relays provide limited magnitude compensation
- SEL relays provide magnitude and phase-shift compensation (SEL-387 considers not only ANSI / IEEE standard connections, but all possible connections)

# Current Magnitude Mismatch

- Current magnitude is transformed (transformer is constant KVA device)
  - $kV_H \cdot I_{\text{high-side}} = kV_L \cdot I_{\text{low-side}}$
  - $I_{\text{high-side}} \neq I_{\text{low-side}}$
- Load tap changer dynamically changes transformation ratio

# Tap Compensation

$$\text{TAP} = \frac{\text{MVA} \cdot 1000 \cdot C}{\sqrt{3} \cdot \text{kV}_{\text{WDG}} \cdot \text{CTR}}$$


where:

C = 1 for wye-connected CTs


C =  $\sqrt{3}$  for delta-connected CTs




# Wye Connection Compensation

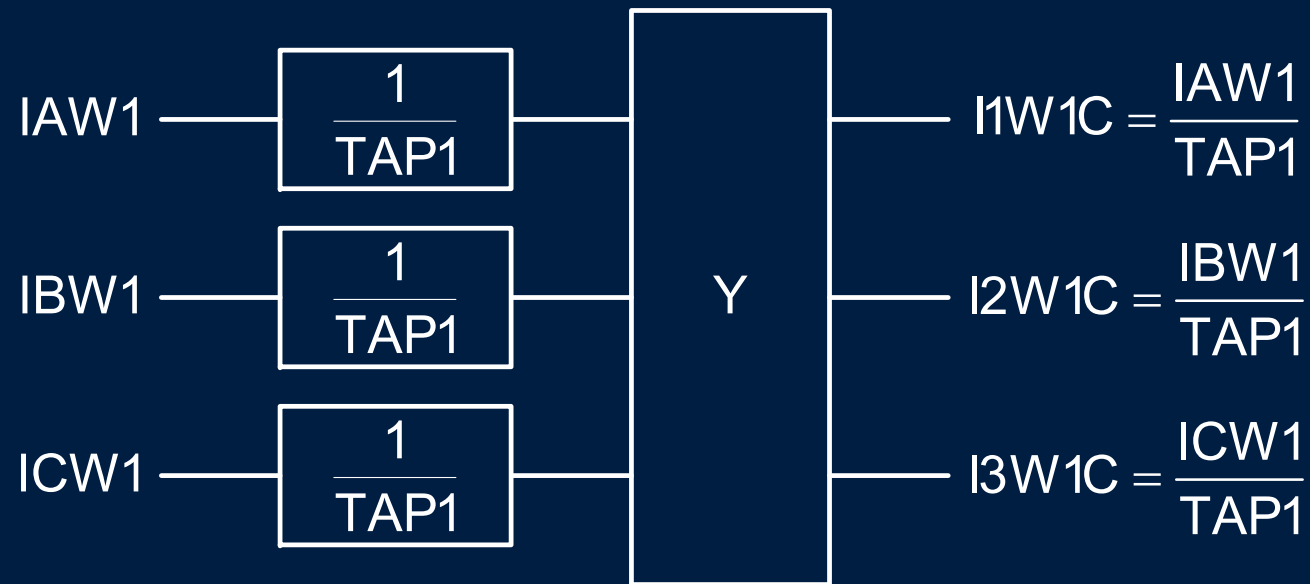

# DAB Connection Compensation

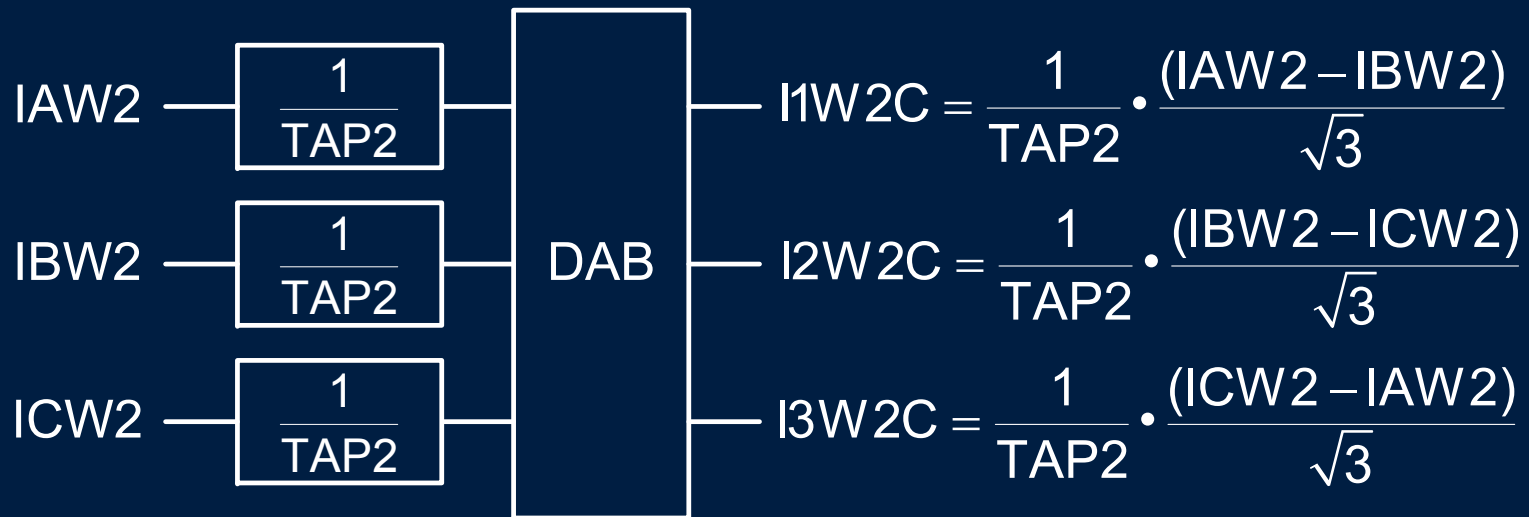


# DAC Connection Compensation

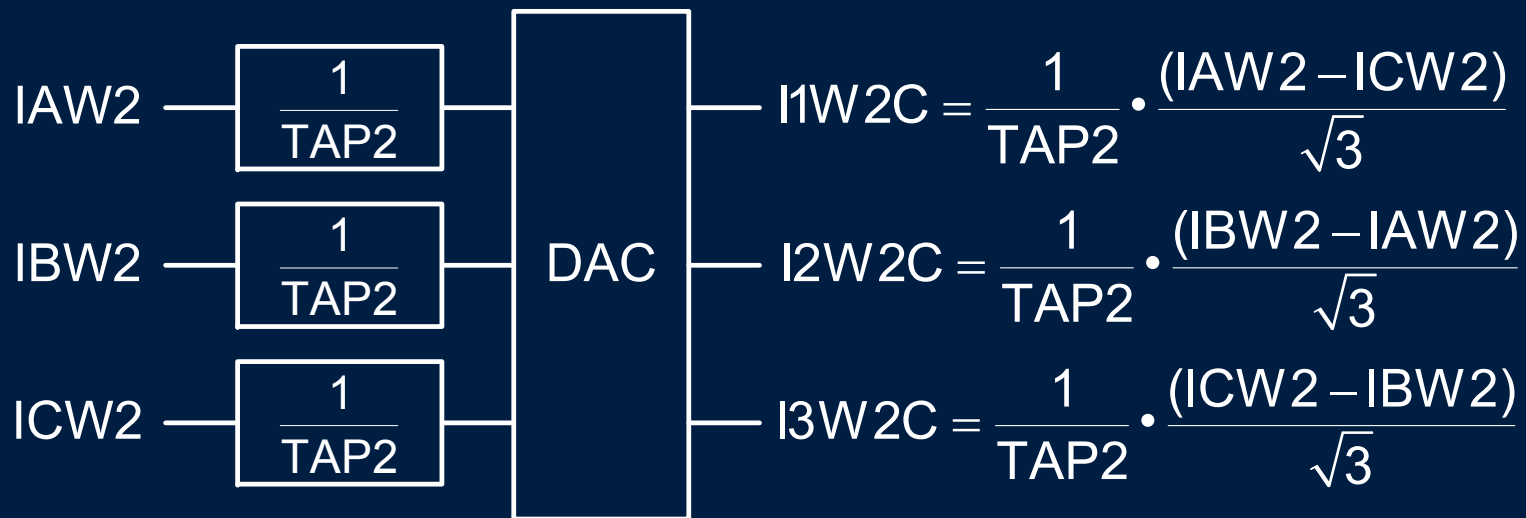


# Compensation for Zero-Sequence Currents

# Why Eliminate Zero-Sequence Current?

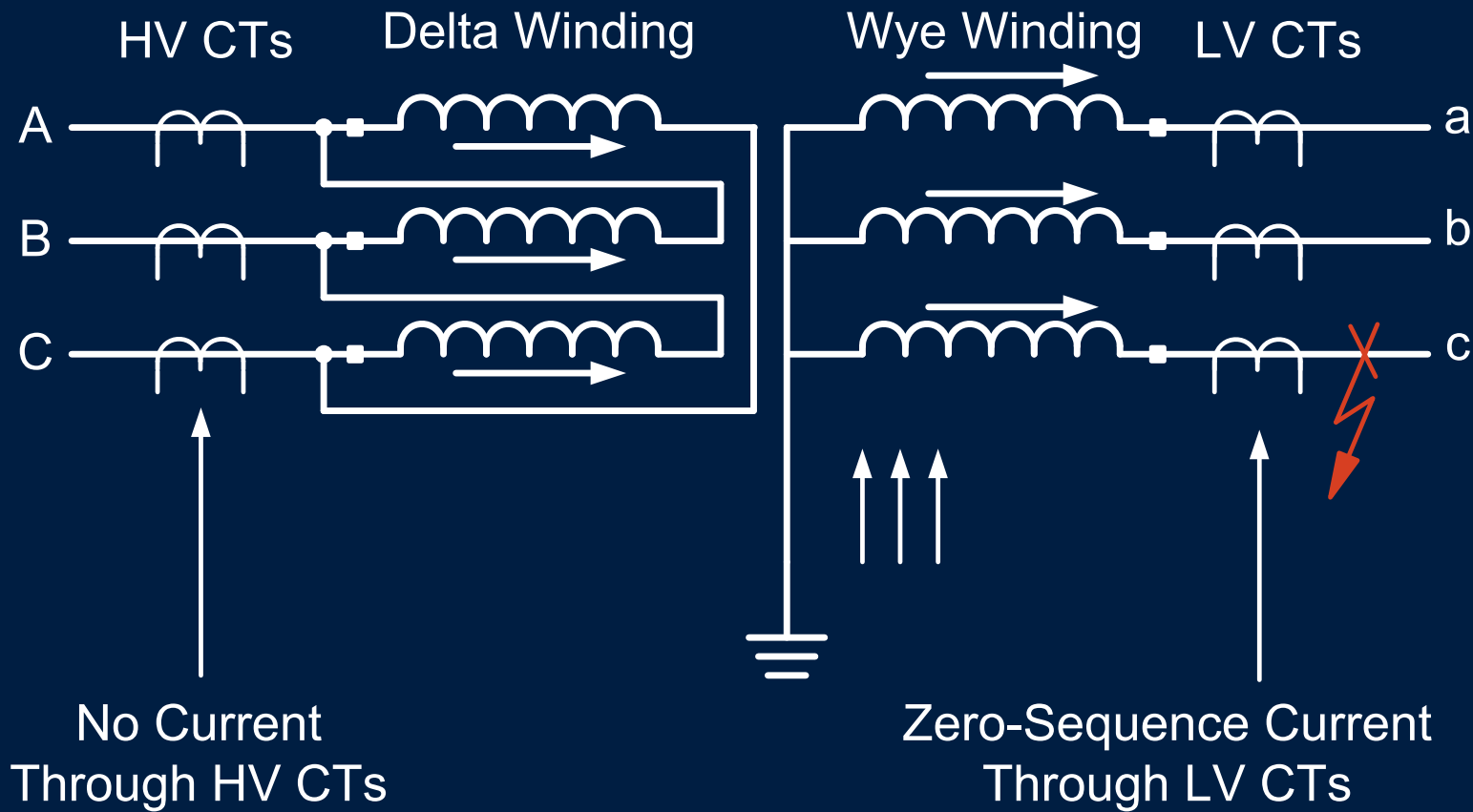

# Removal Via Delta Connection


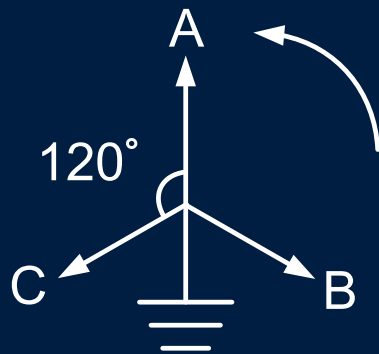


$$I_a = I_1 + I_2 + I_0$$

$$I_b = a^2 I_1 + a I_2 + I_0$$

$$I_a - I_b = I_1 + I_2 + I_0 - (a^2 I_1 + a I_2 + I_0)$$
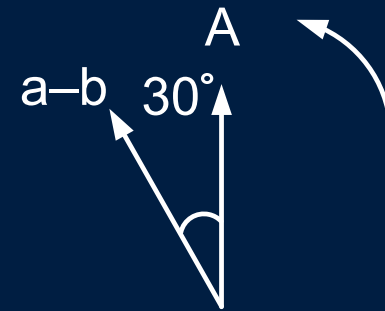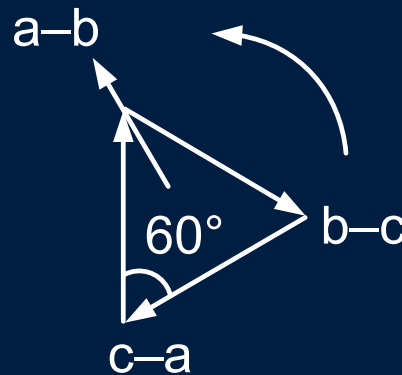
$$= I_1(1 - a^2) + I_2(1 - a) + (I_0 - I_0)$$




Zero-Sequence  
Current Eliminated

# Restrained Differential Element

# Differential Protection Principle


## Unequal CT Performance

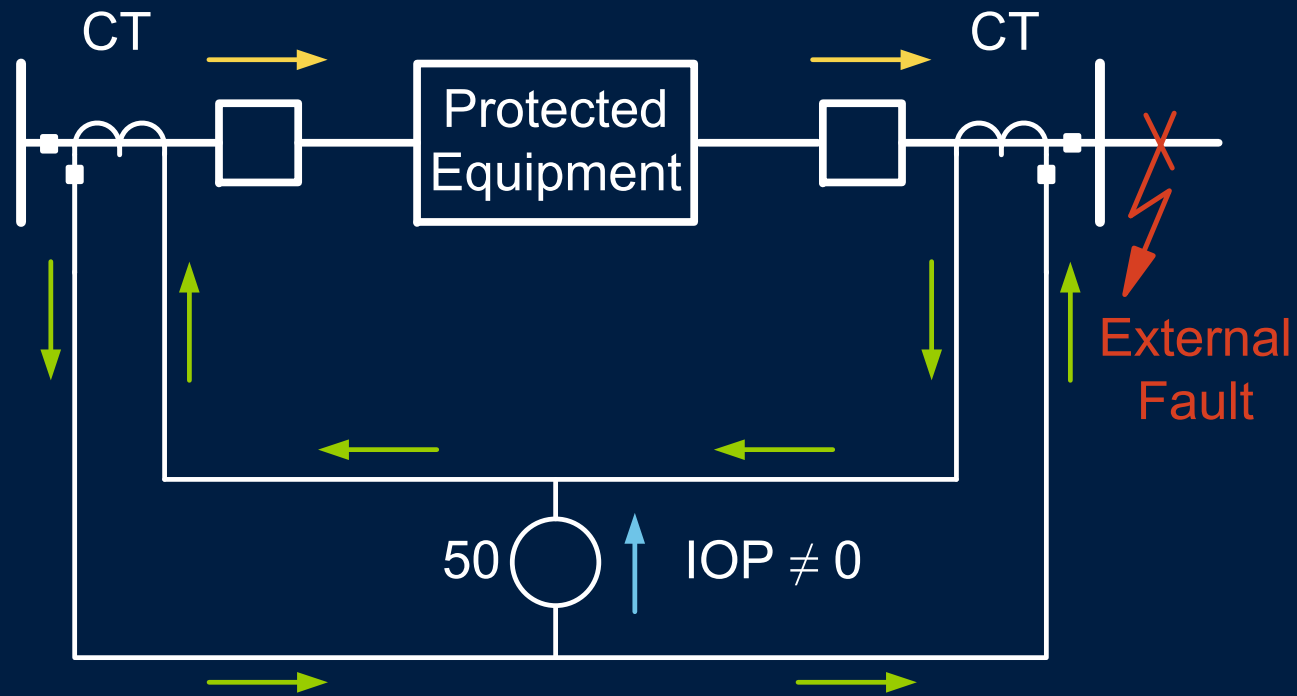

CT saturation and CT ratio error



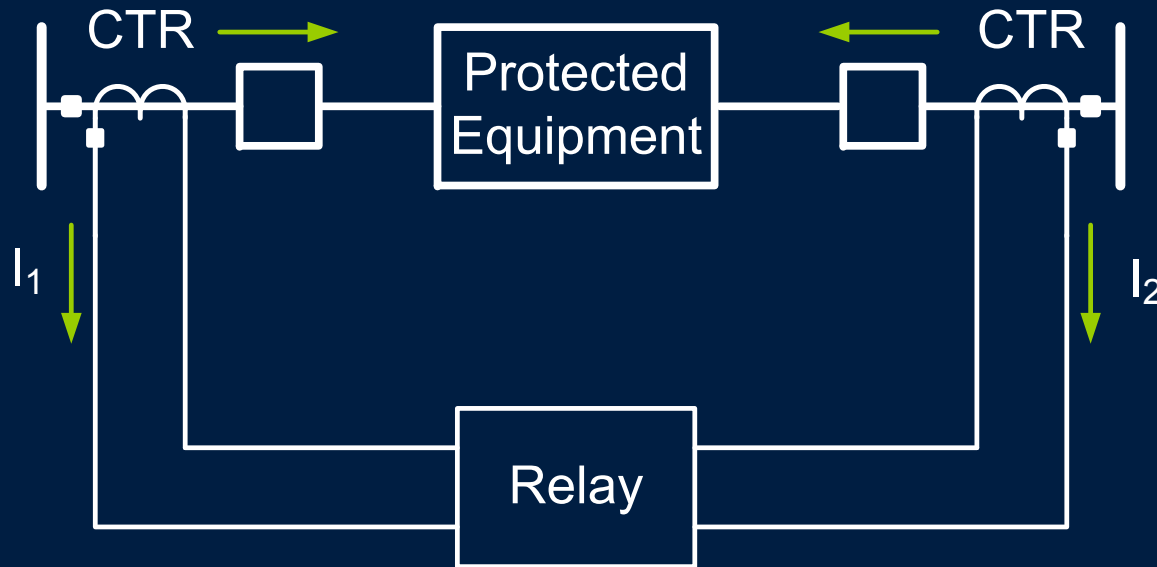
# Percentage Differential Protection Principle




$$IOP = |\bar{I}_1 + \bar{I}_2|$$

$$IRT = 0.5 \cdot (|\bar{I}_1| + |\bar{I}_2|)$$

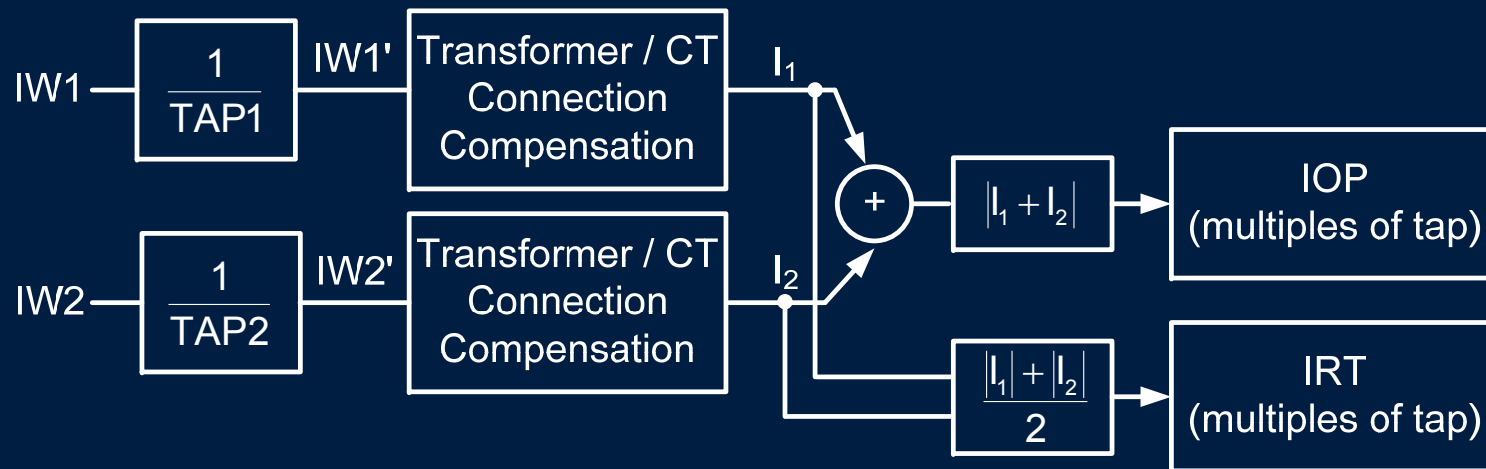
# Differential Element Operate and Restraint Quantities


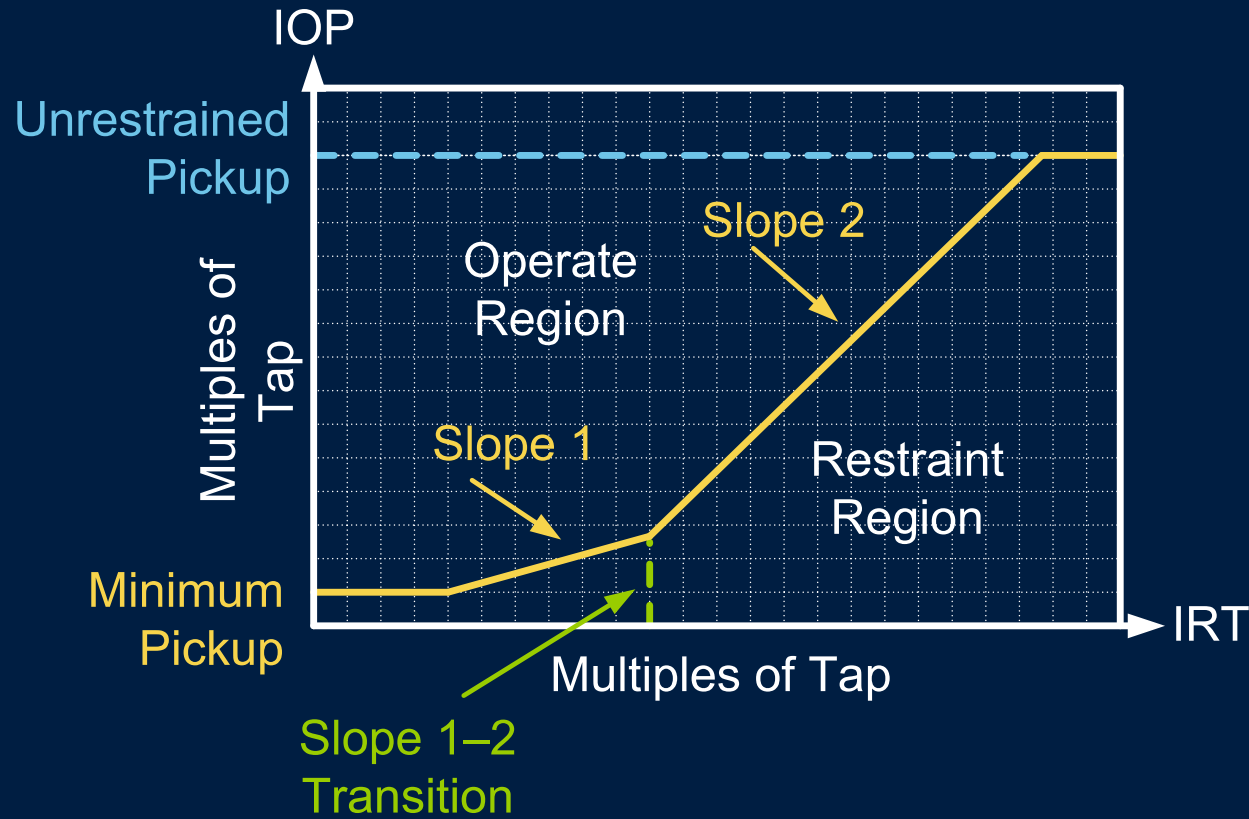
# Percentage Restraint Differential Characteristic



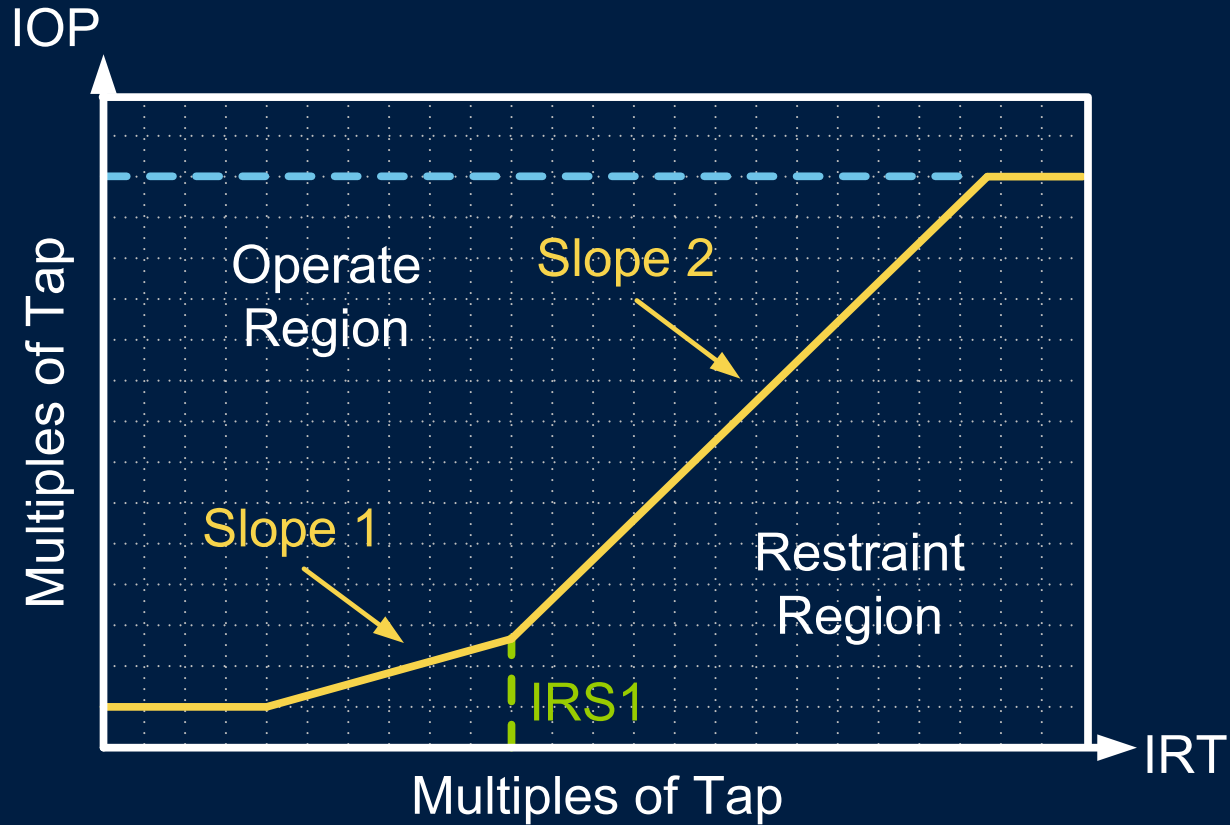
# Percentage Restraint Differential Characteristic




# Transformer Energization

# C-Phase Inrush Current

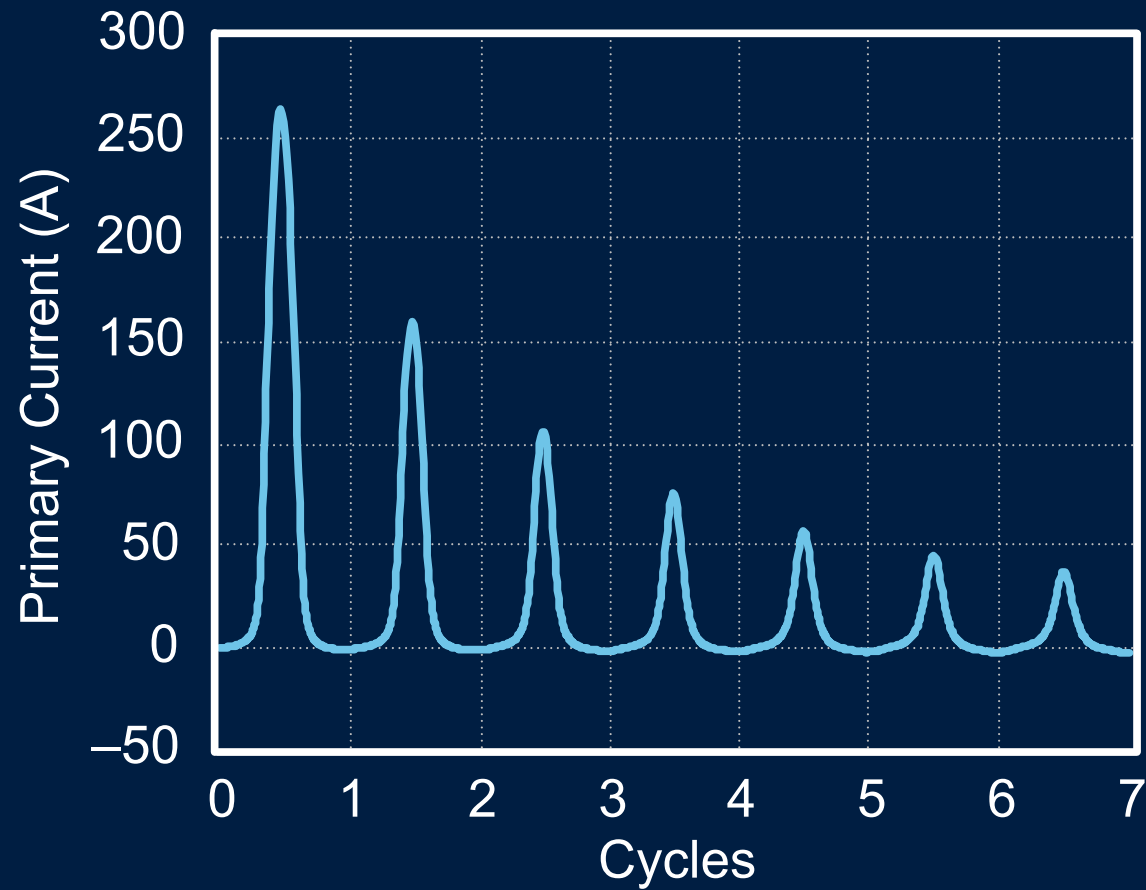

# Inrush Current

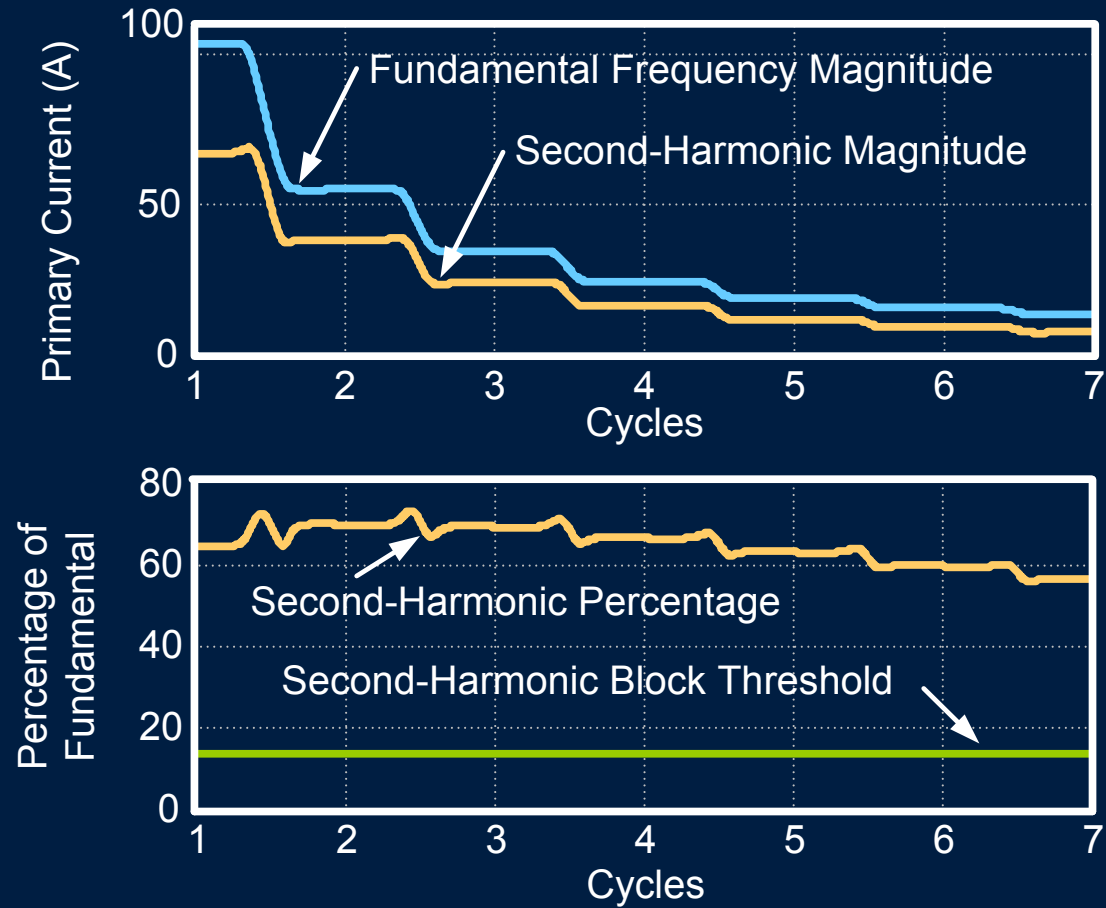


# Discriminating Internal Faults Versus Inrush Conditions


- Harmonic blocking
- Harmonic restraint
- DC blocking



# DC Blocking

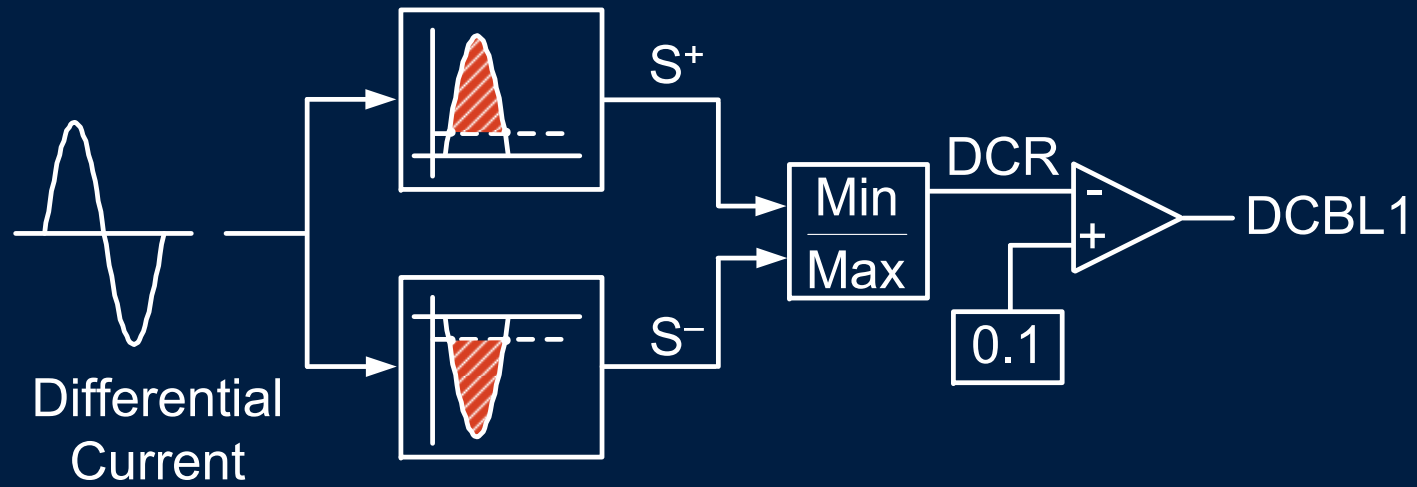

# DC Blocking

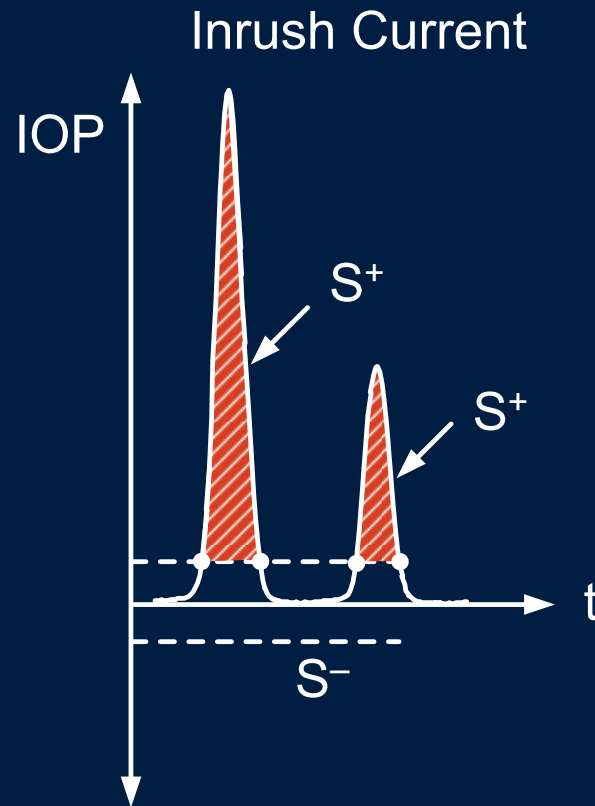

$$S^+ = 1$$


$$S^- = 0$$

$$0/1 = 0$$

$$0 < 0.1$$

DCBL1 is asserted

# DC Blocking

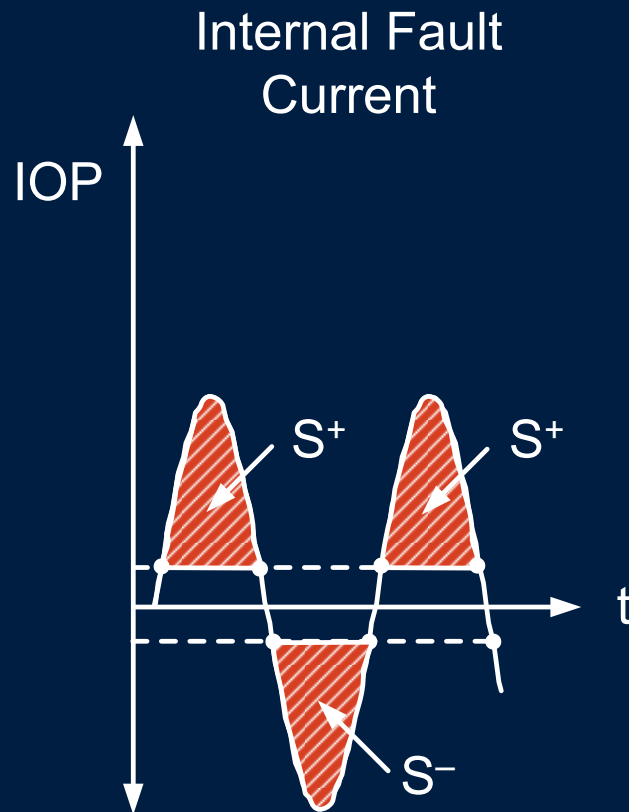

$$S^+ = 1$$


$$S^- = 1$$

$$1/1 = 1$$


$$1 > 0.1$$

DCBL1 is not asserted

# Inrush Conditions (Blocking)

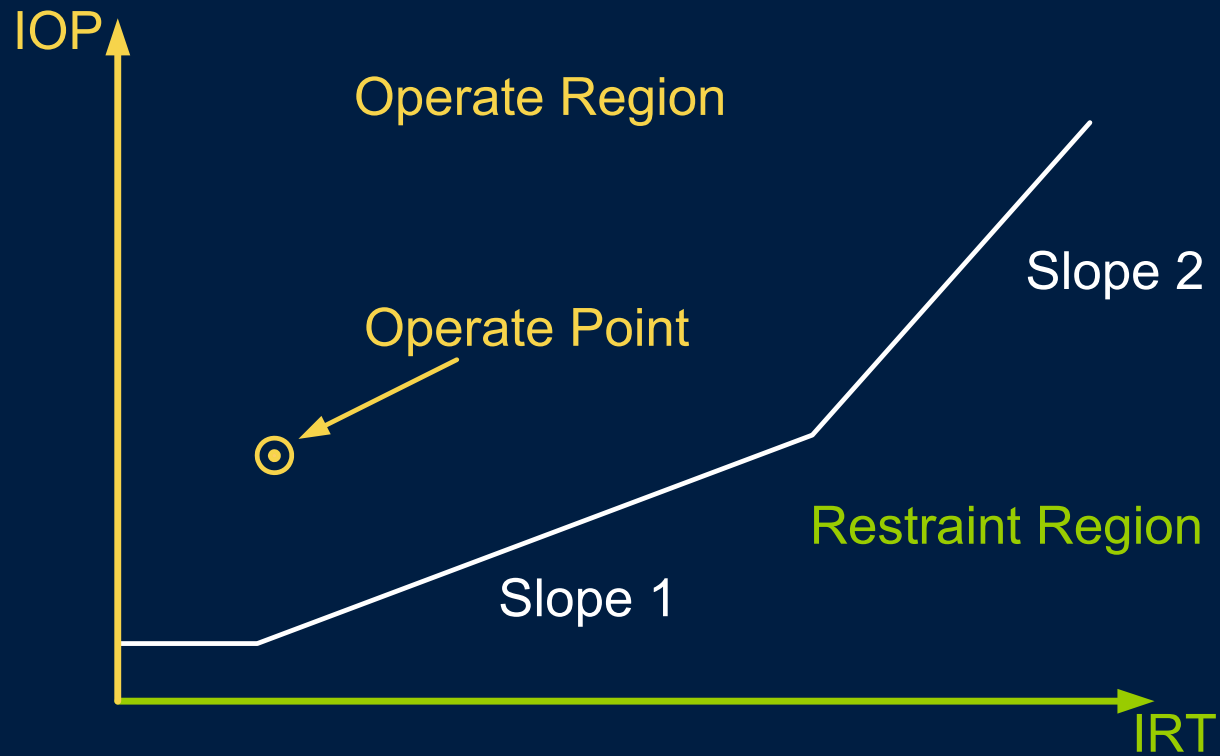

# Inrush Conditions (Restraint)

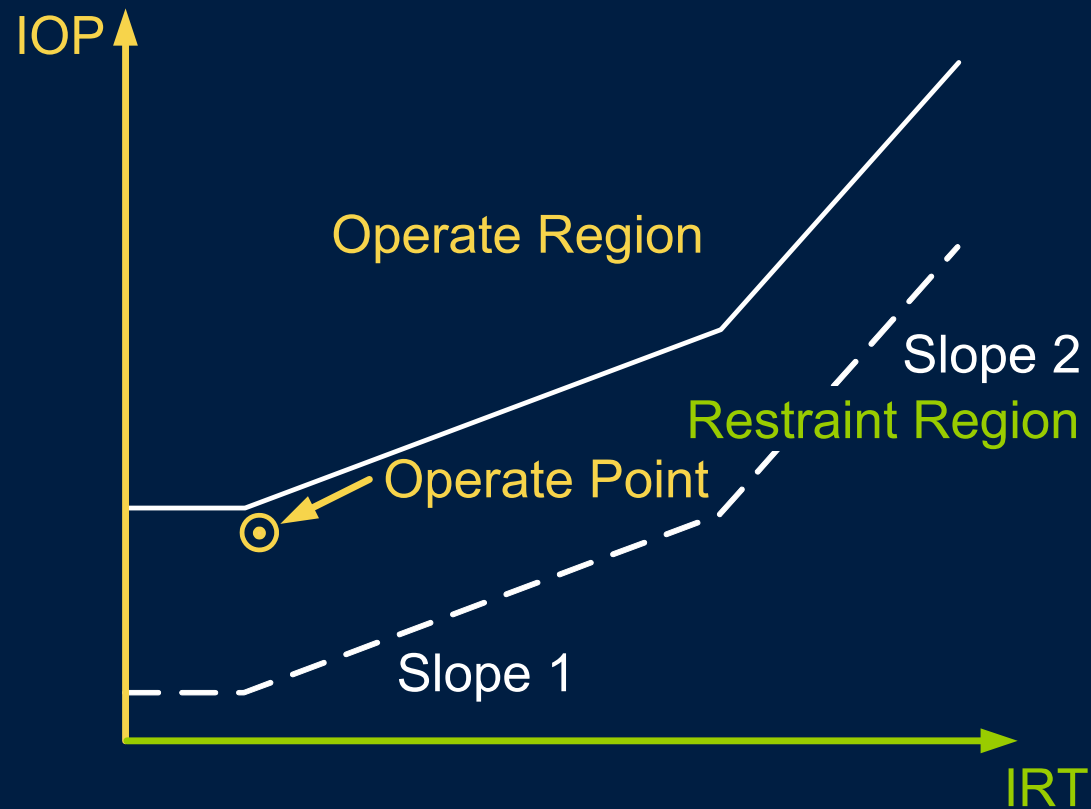

# Unrestrained Differential Element


## Unrestrained Element

- Element instantaneously trips on magnitude of differential current
  - No percentage restraint
  - No harmonic block
- CT saturation includes harmonics

# Transformer Overexcitation



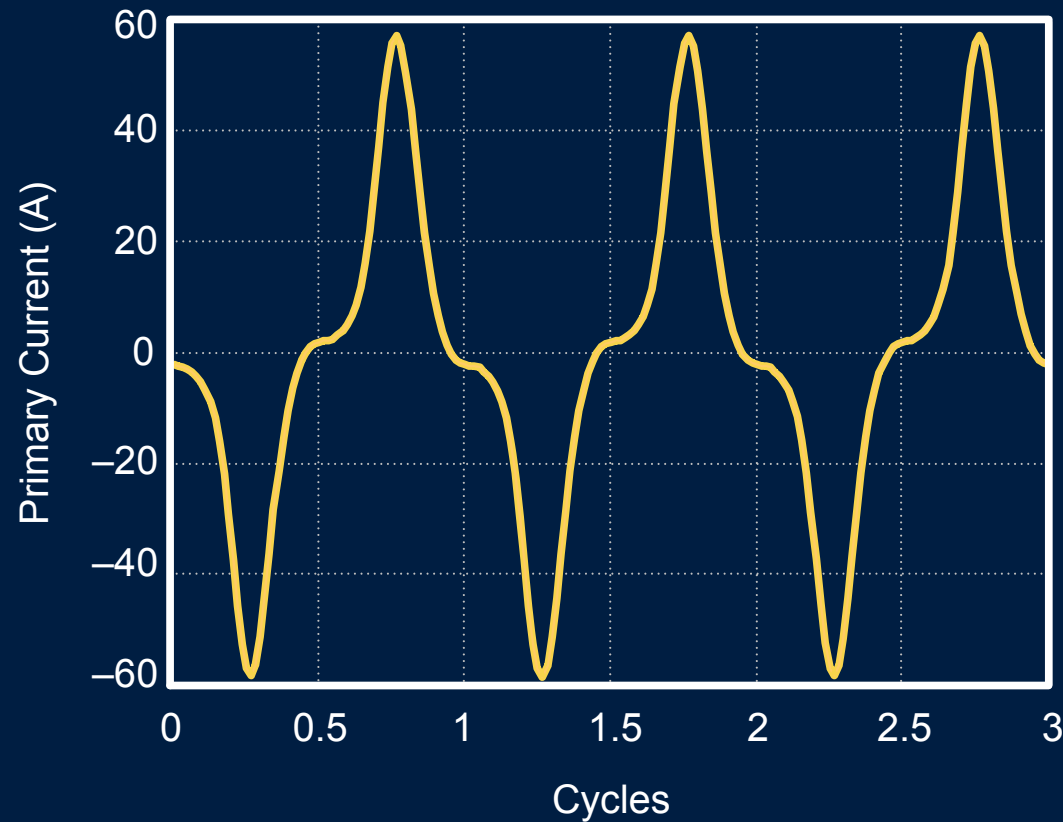
# Excitation Current From Testing 150 Percent Overvoltage



# Fifth-Harmonic Content in Excitation Current


Frequency Component	Magnitude (primary A)	Percent of Nominal
Fundamental	22.5	52.0
3rd	11.1	26.0
5th	4.9	11.0
7th	1.8	4.0

# Excitation Current Harmonics

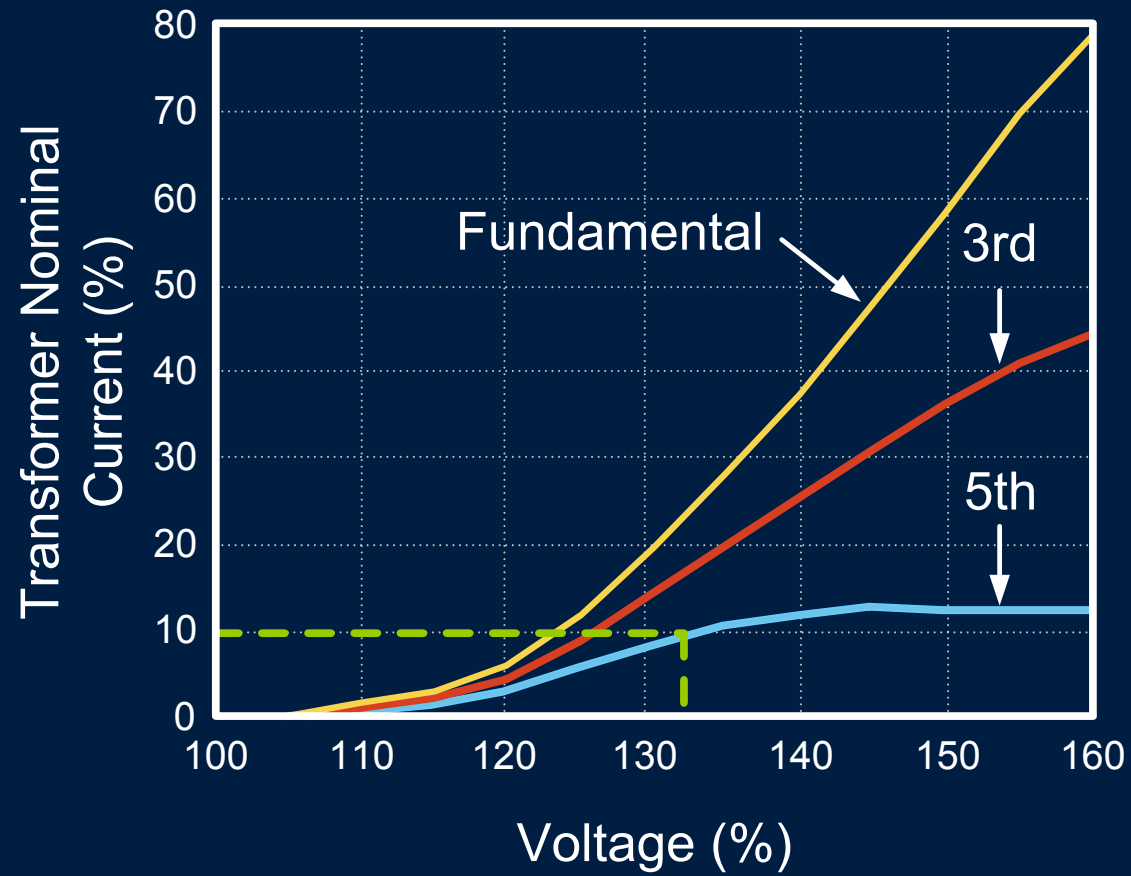


# Application Considerations

# Paralleling CTs on Restraint Input

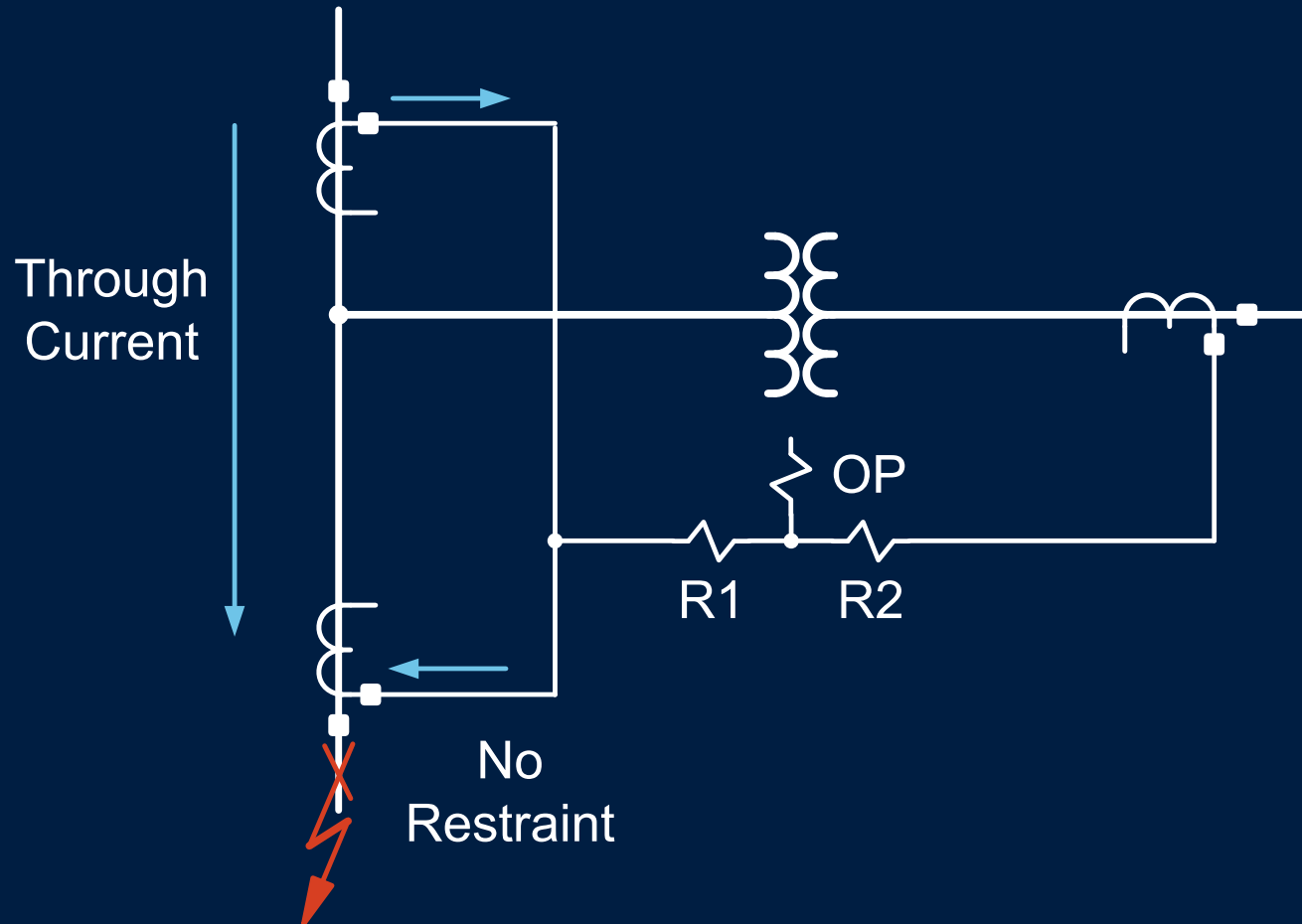


# Paralleling CTs on Restraint Input

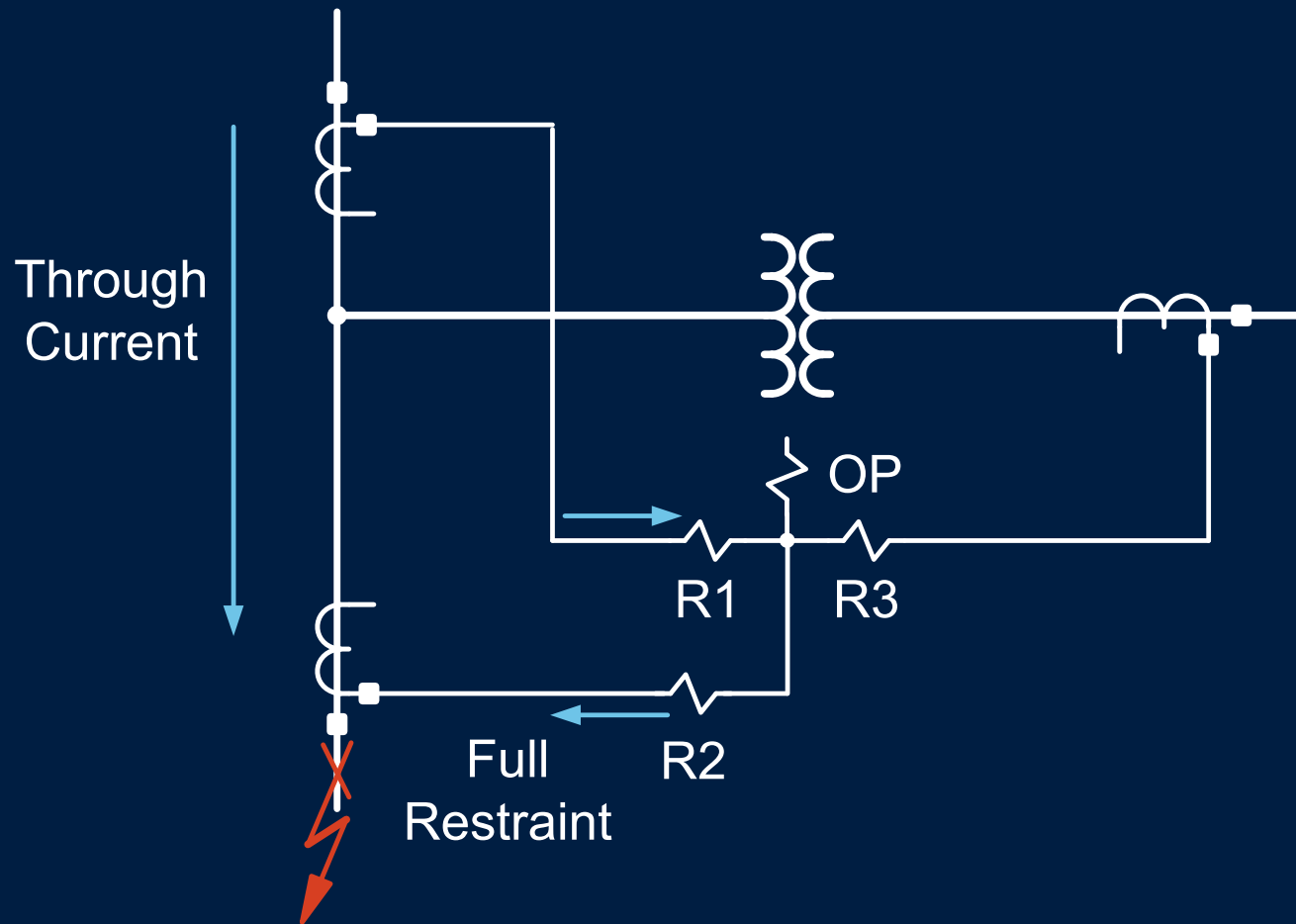

# Paralleling Transformers

## Sympathetic Inrush

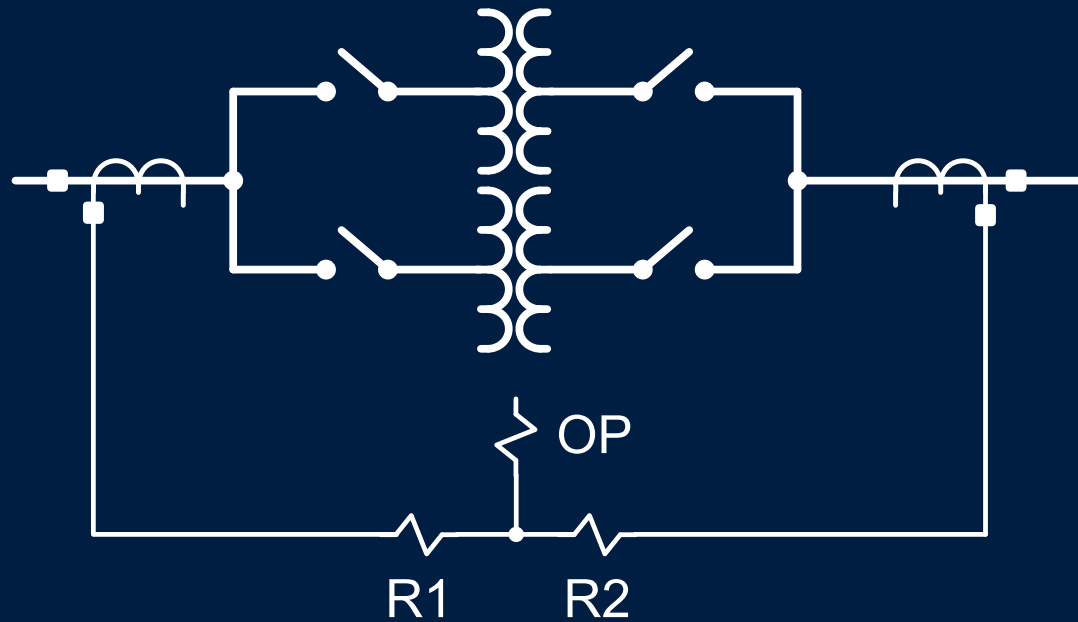


# Setting Taps for Three-Winding Transformers

- Know that third winding may not be rated at same MVA as main windings
- Set taps on multirestraint relay
  - Work through matching taps in pairs
  - Be sure to use same MVA base for each tap calculation




# Restricted Earth Fault (REF) Protection

# Protect Windings Close to Neutral

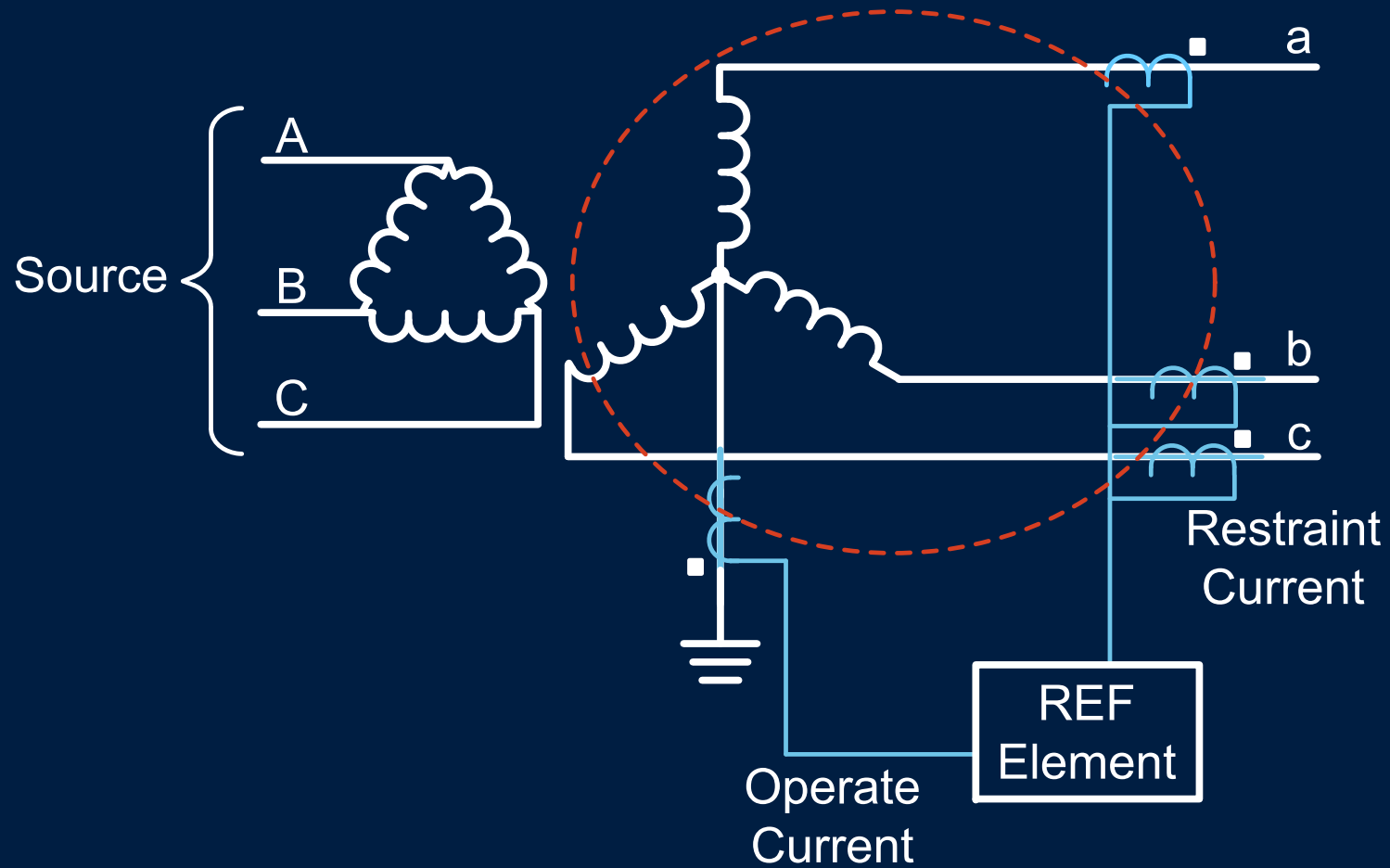
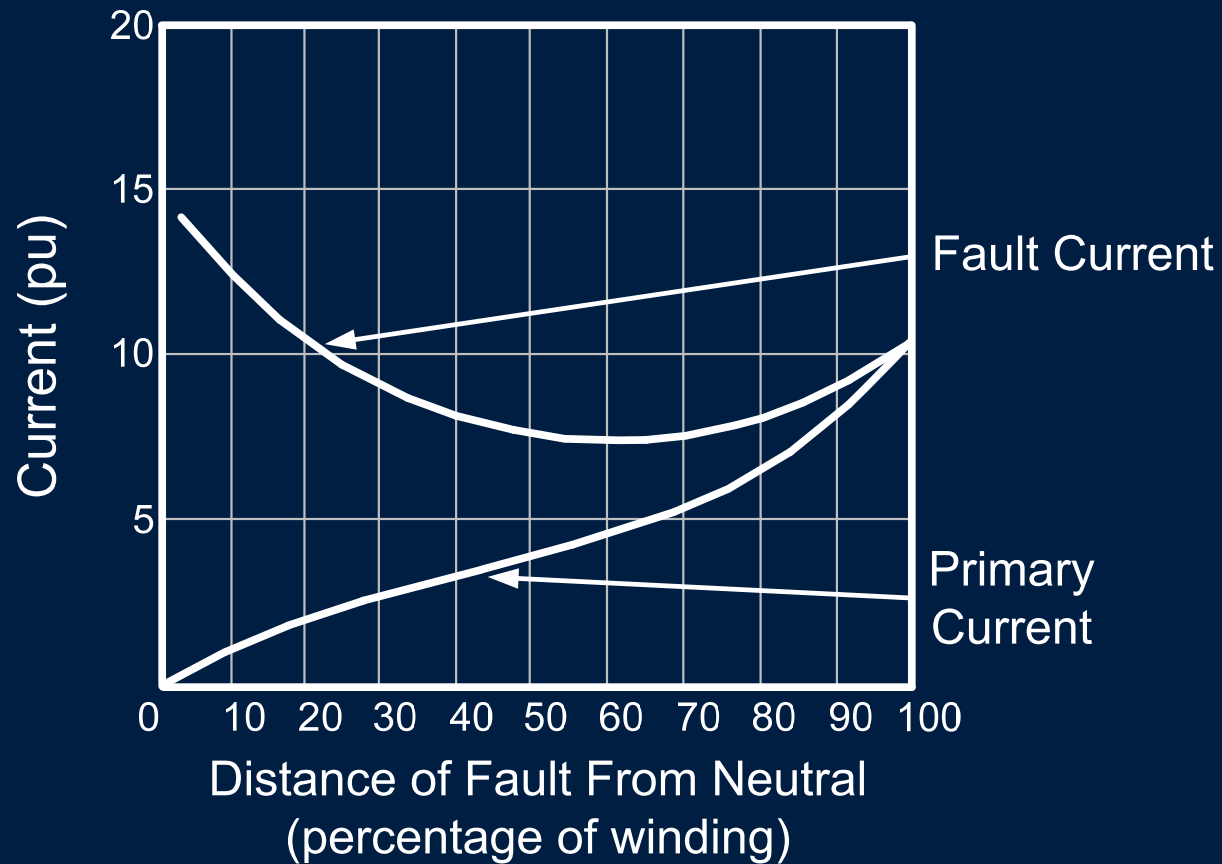
# Protection Basics – Why Use REF Protection?




# Prevention Before Protection


- Thermal model
- Through-fault monitoring




# What Causes Transformer Overheating?

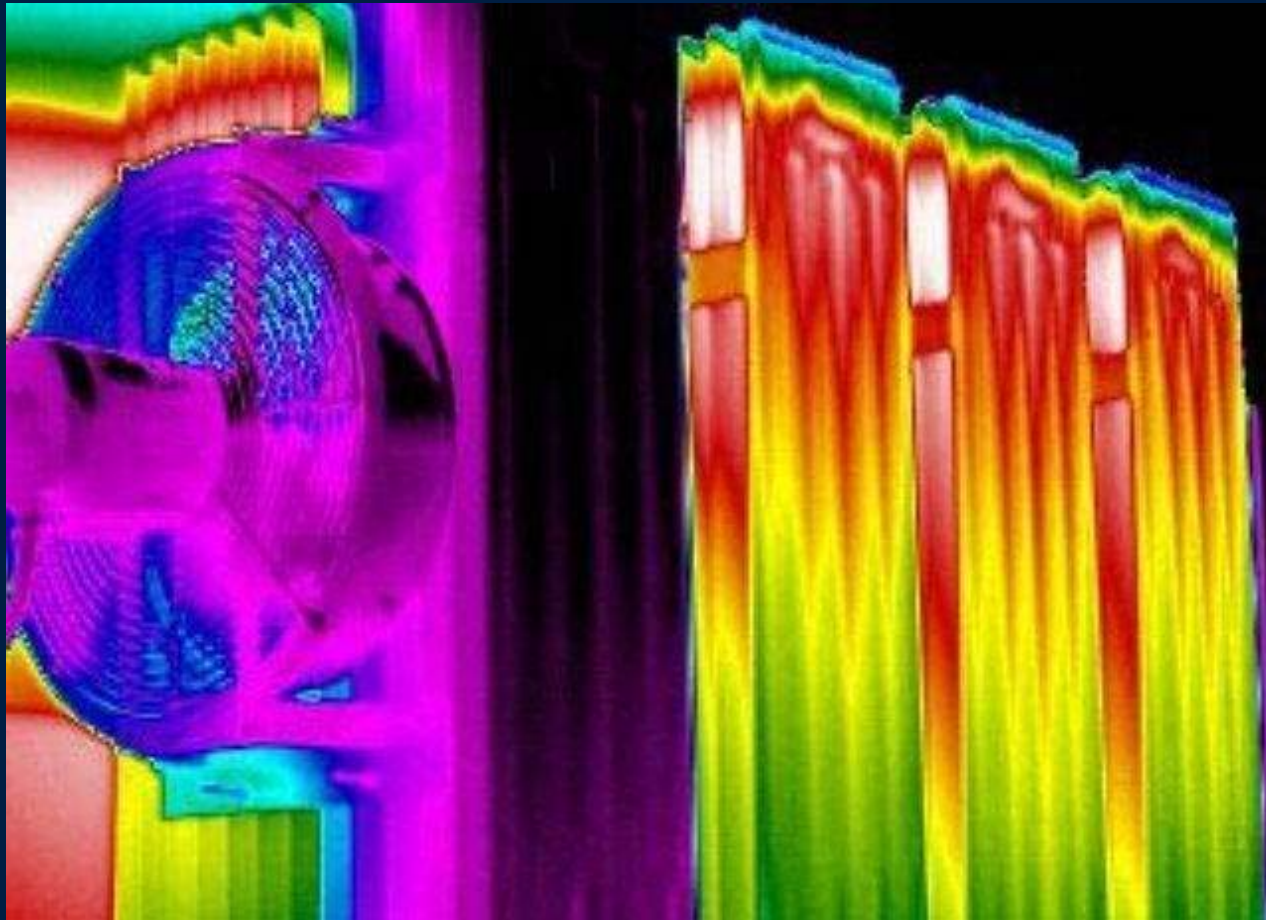


# What Does Overheating Do?

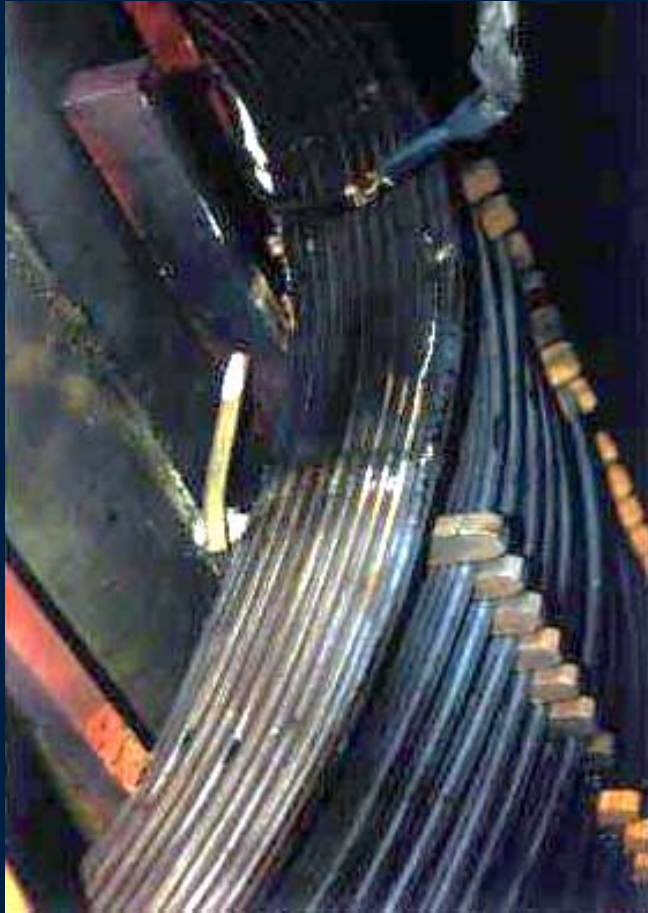

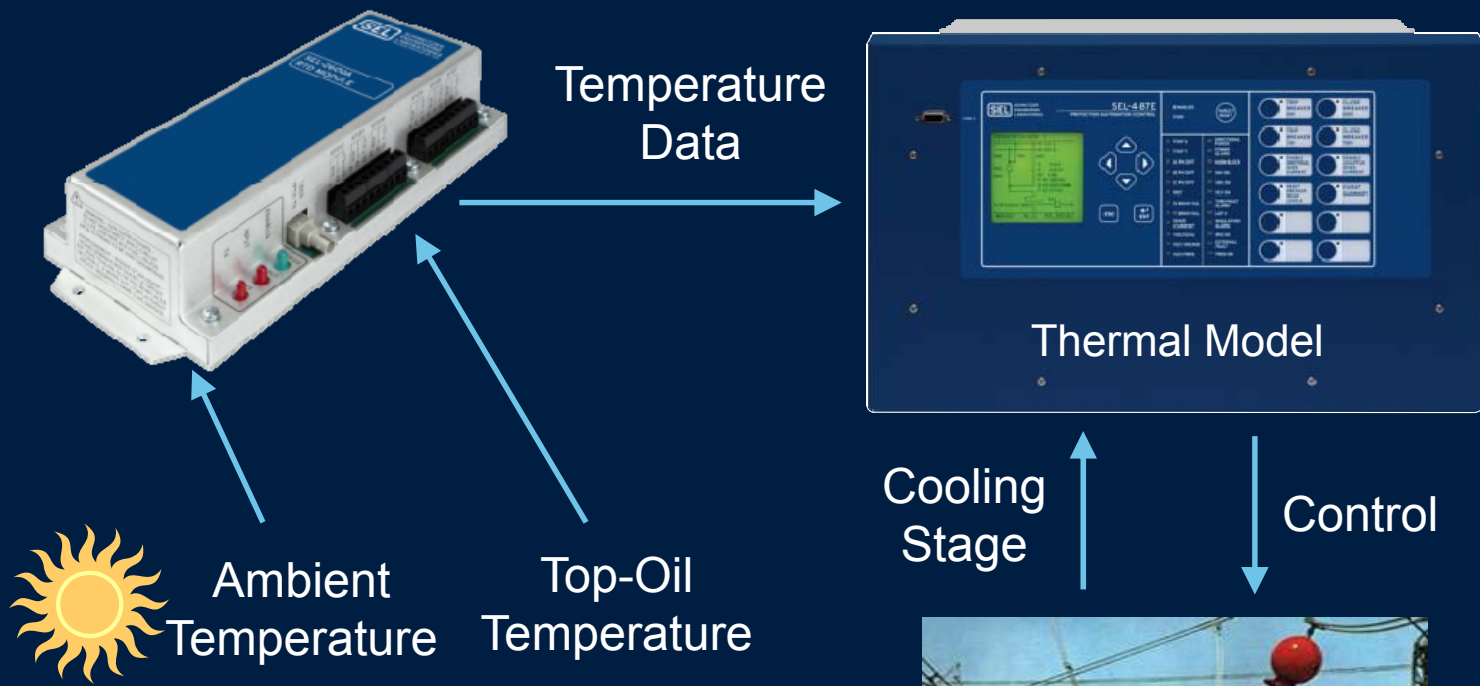


# Prevention Basics – Control Fan Banks

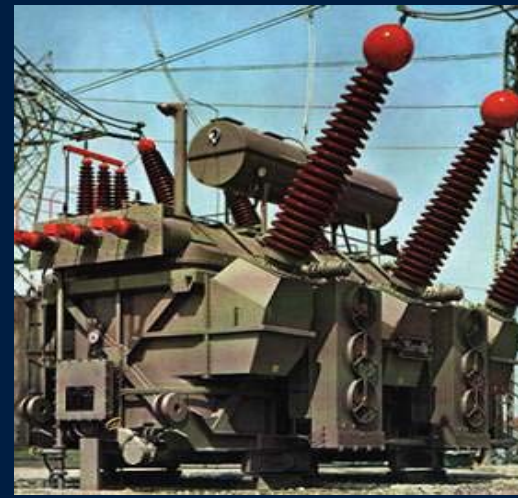




# Why Enable Through-Fault Monitoring?

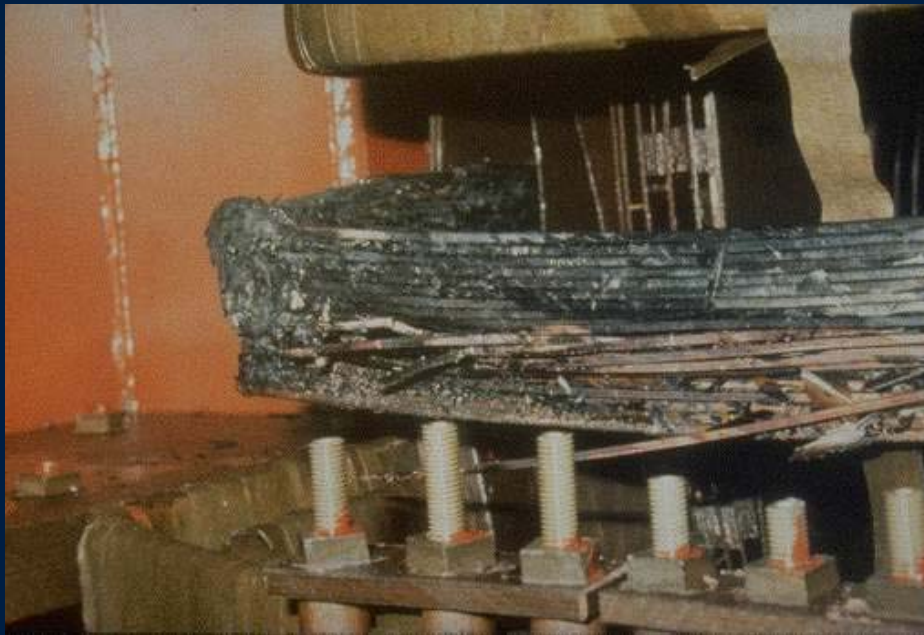



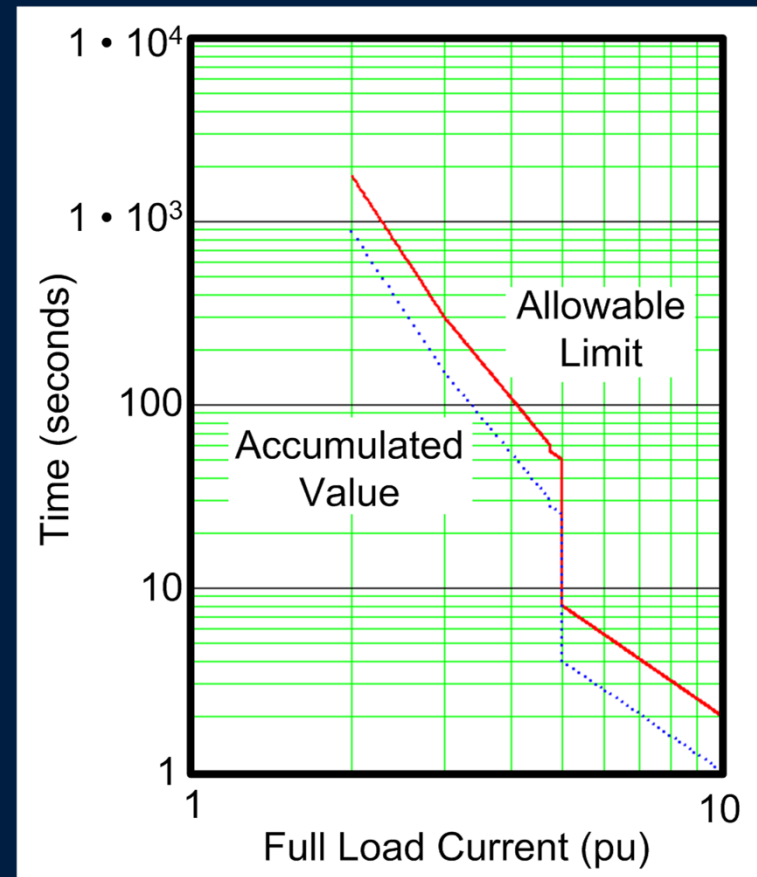
# Track Through Faults Transformer Has Experienced


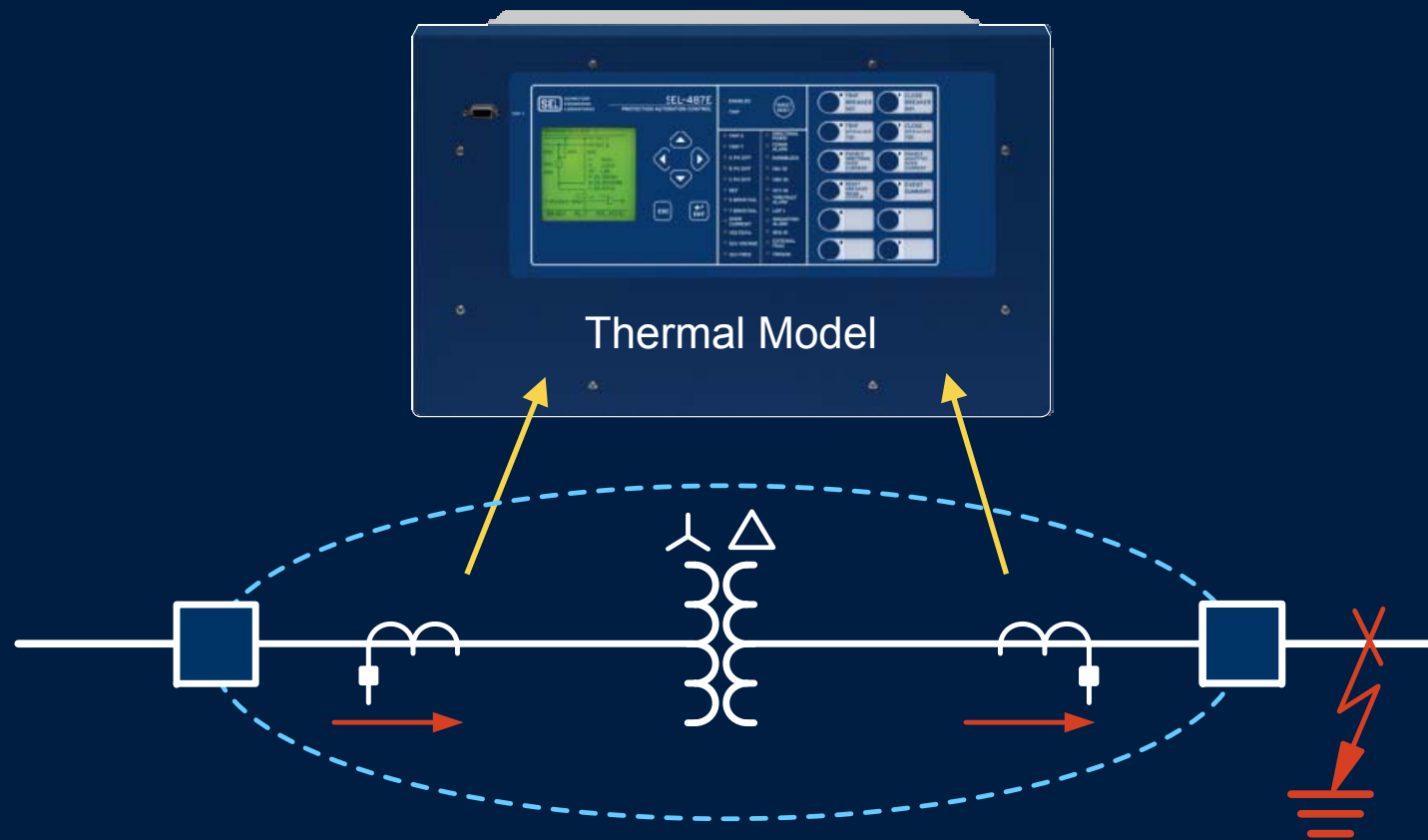
# Prevention Basics – Enable Through-Fault Monitoring



Questions?

